

ELEN30013 Electronic System Implementation



THE UNIVERSITY OF
MELBOURNE

Week 6/1: Review + Driving Actuator + Introduce to Signal Conditioning





Presenter: Jie (Jack) Li

Email: jie.li@unimelb.edu.au

Sep 2016




Week 3 Workshop Review: LTspice Simulation

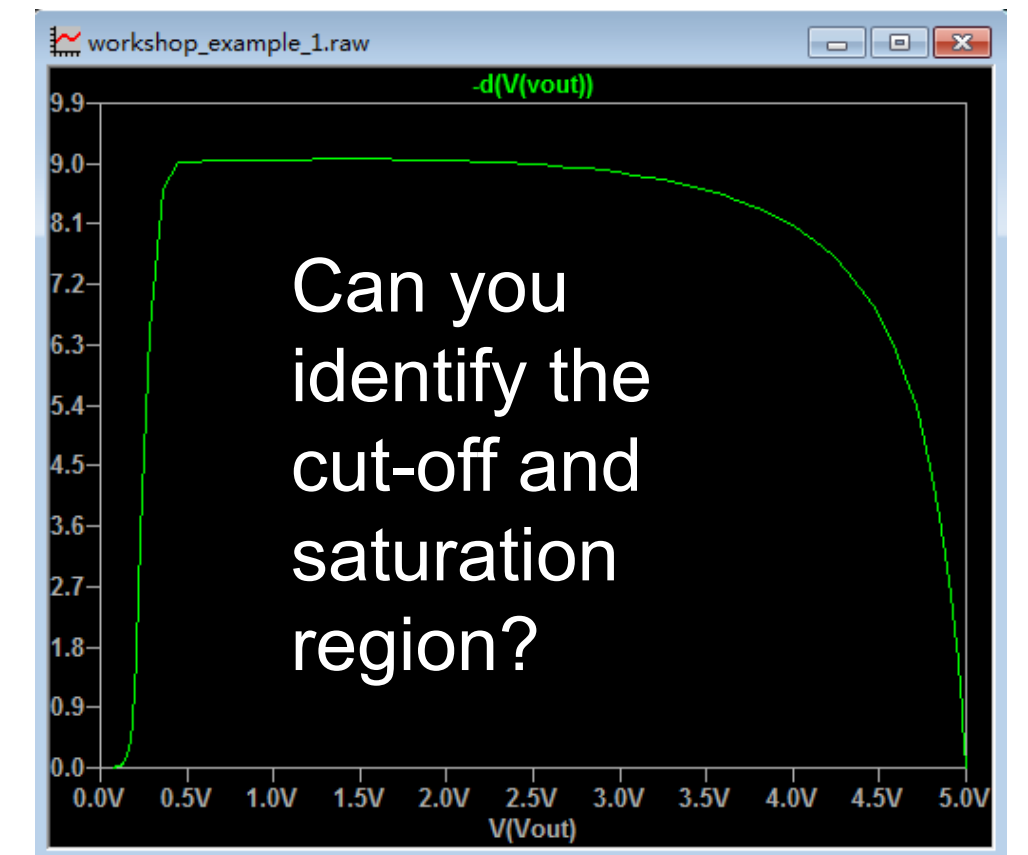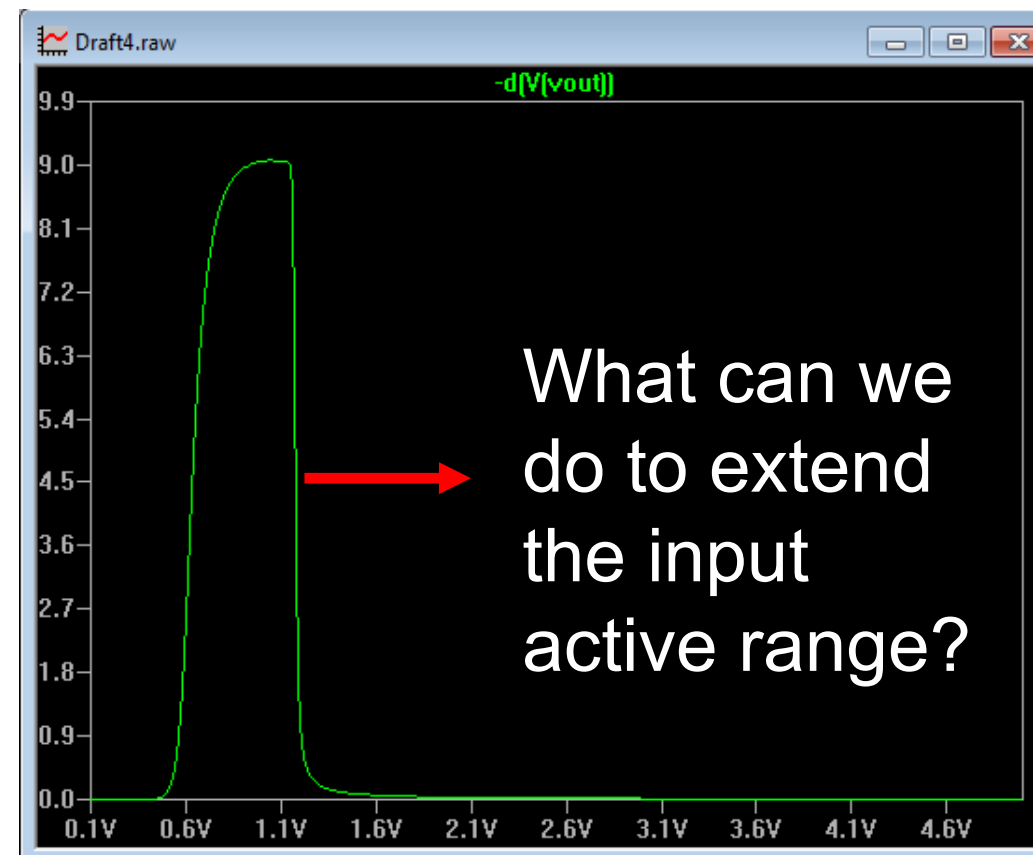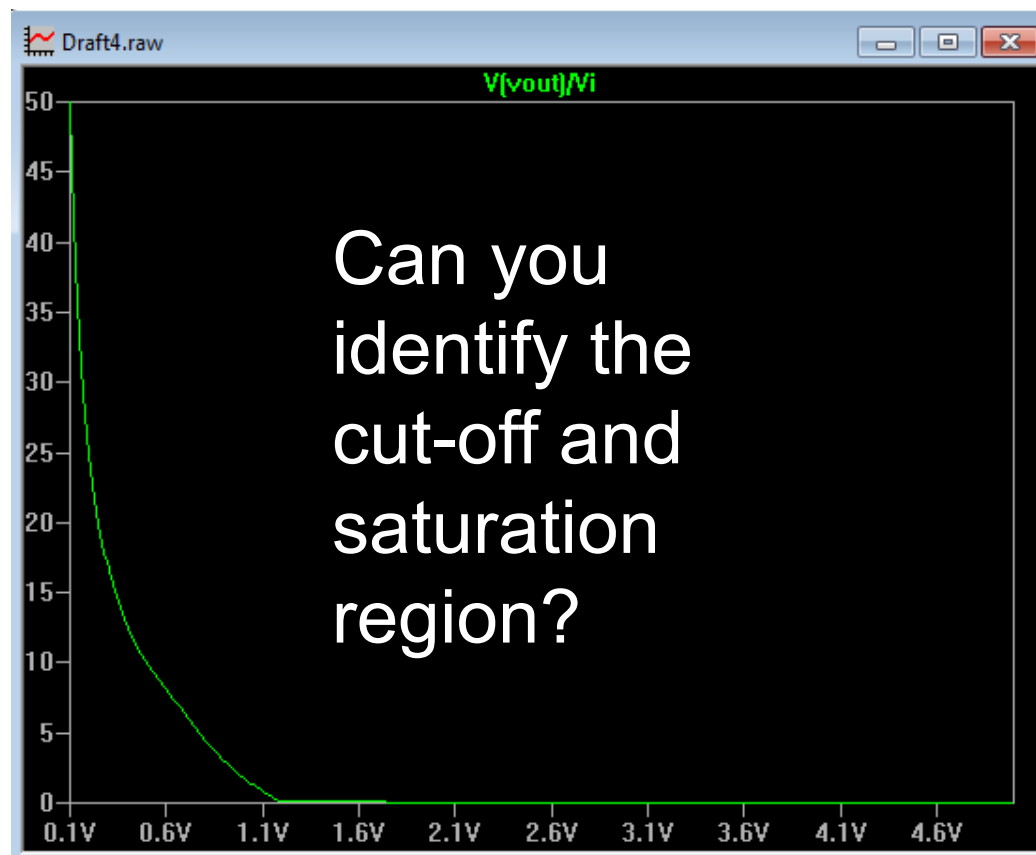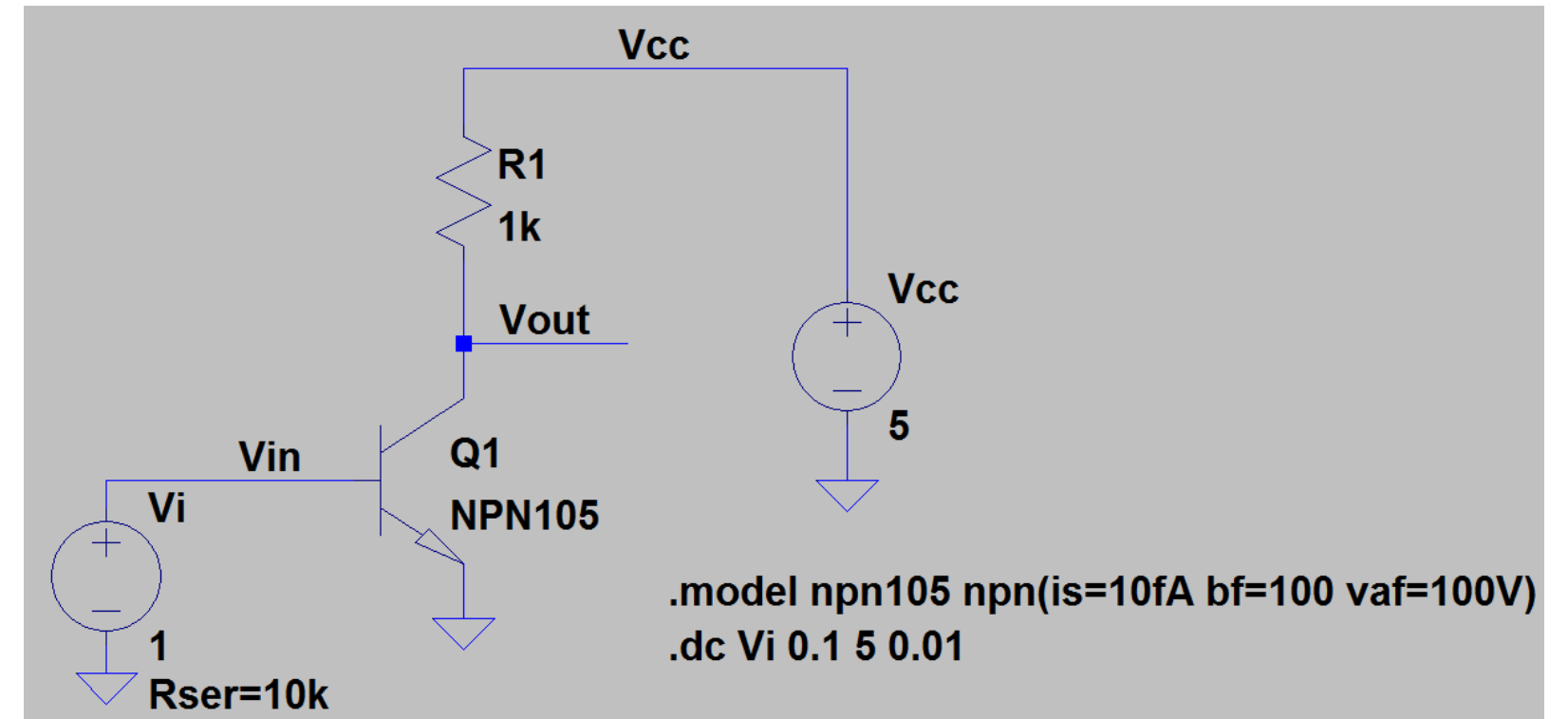- DC Analysis
 - Identify the operation conditions for different mode
 - ➔ Design circuit to meet design requirement




Week 3 Workshop Review: LTspice Simulation

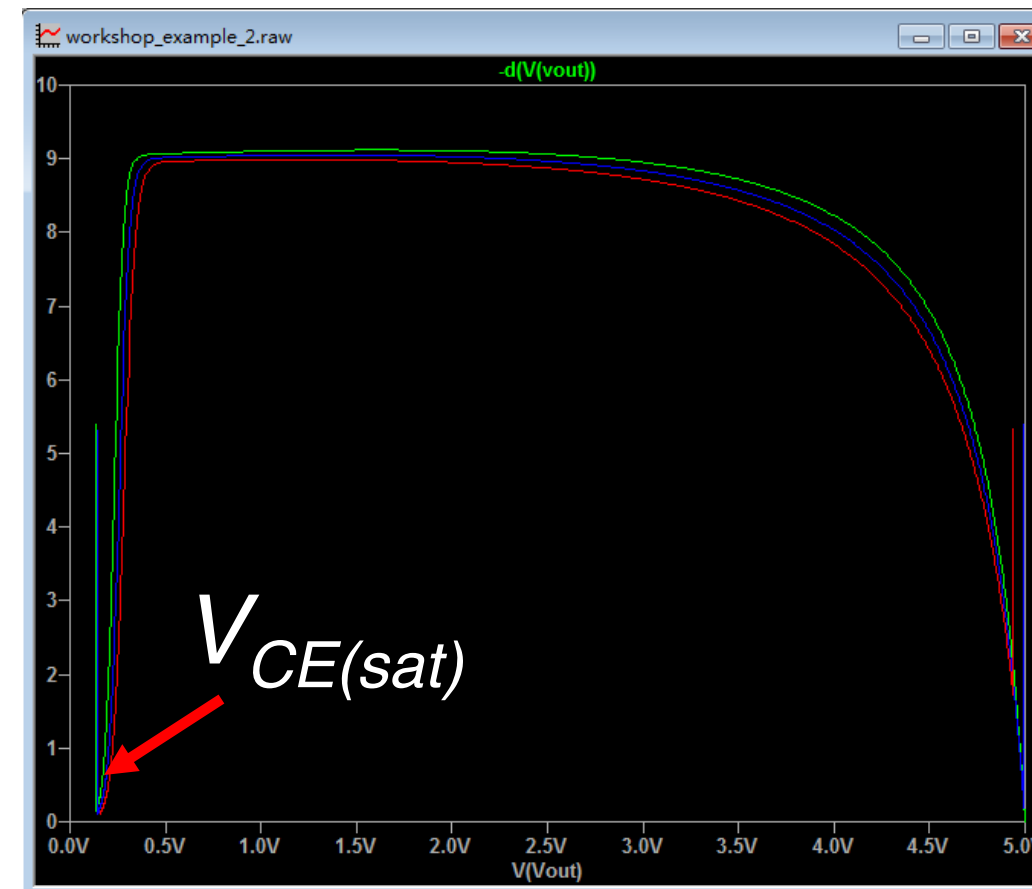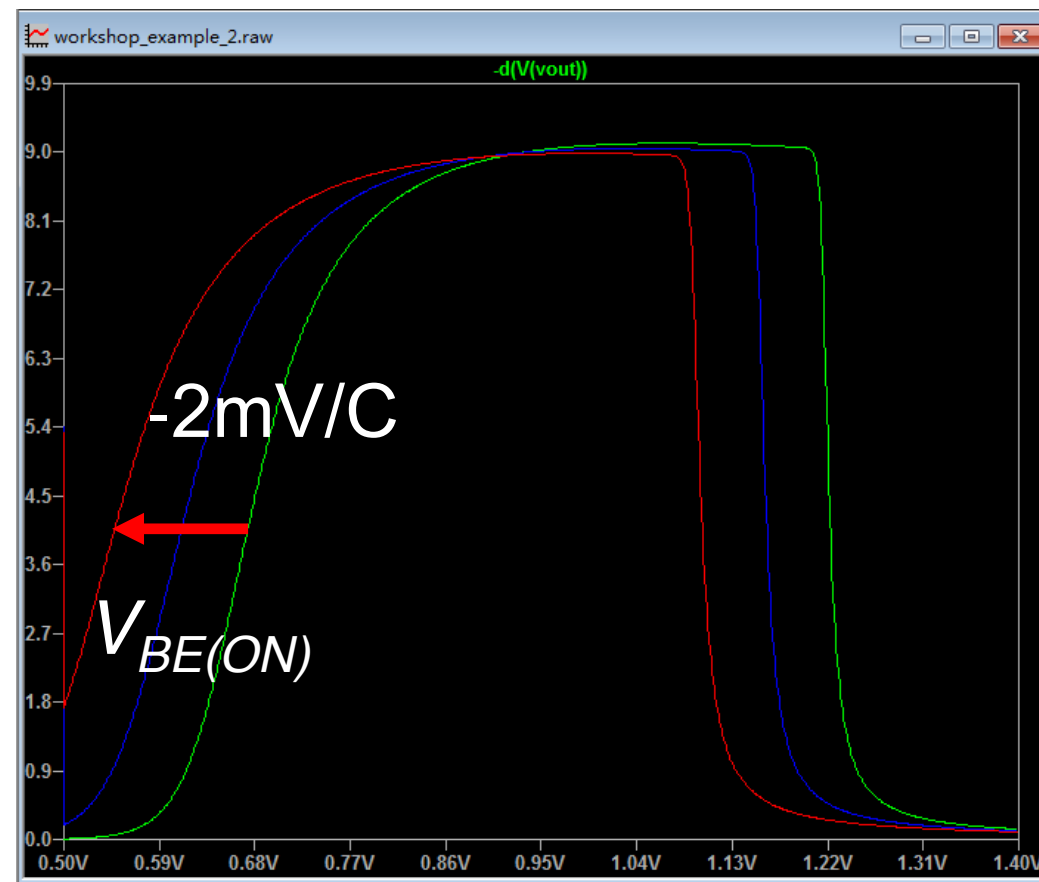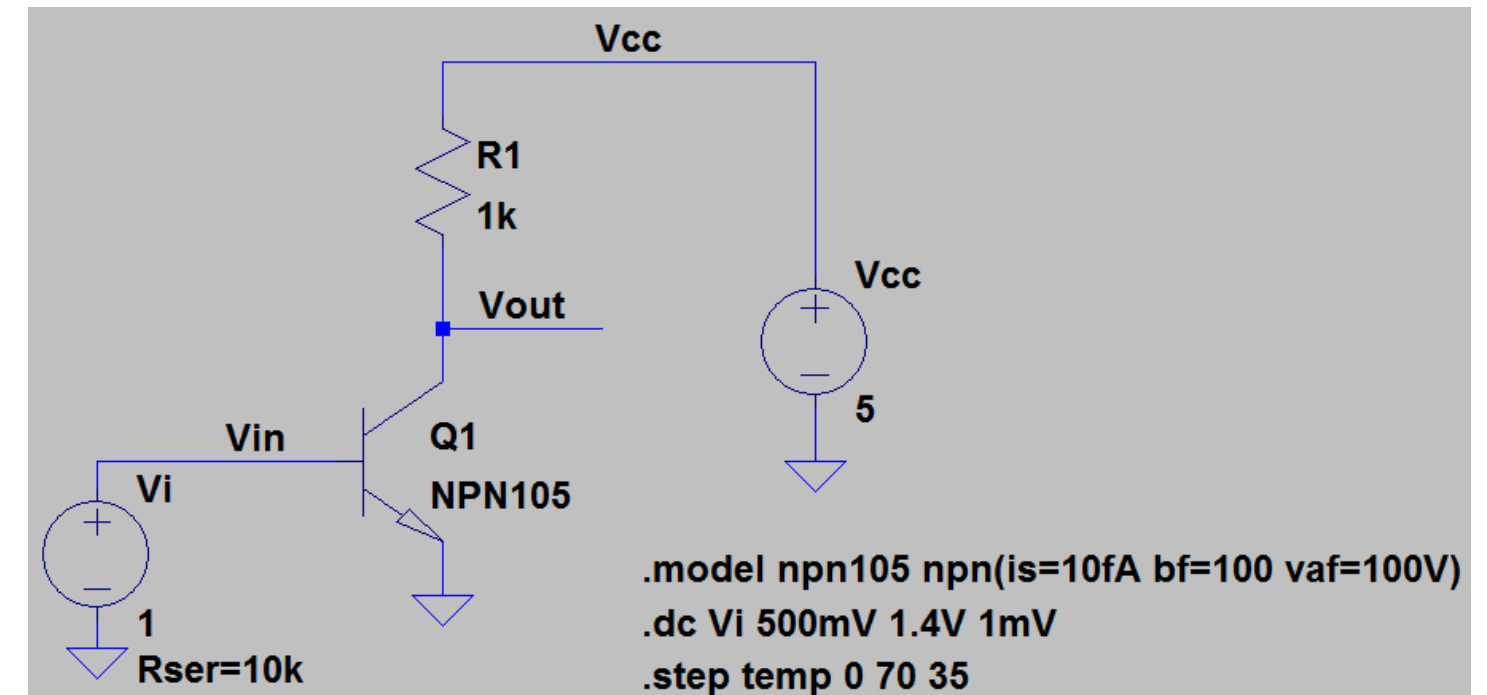- Temperature variation impact
 - Notice the variation and taken it into your design calibration



Week 3 Workshop Review: LTspice Simulation

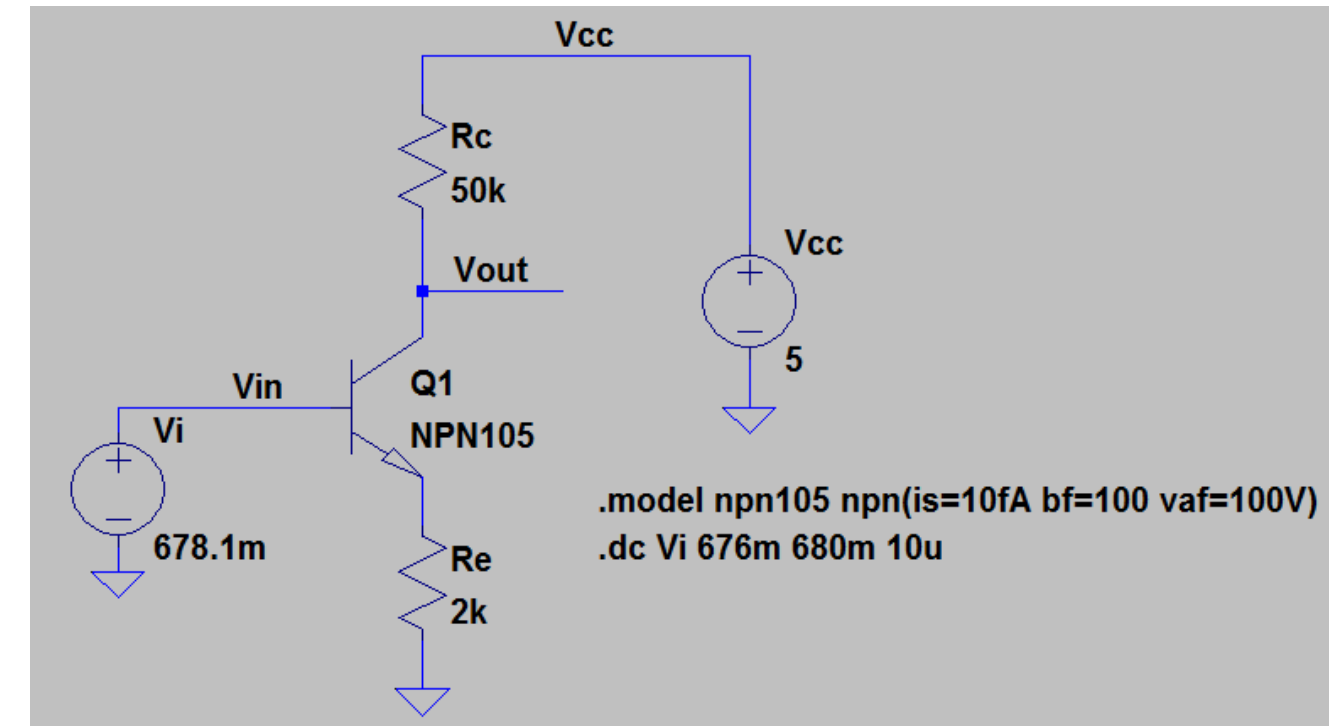- Why Emitter Degeneration?
 - Gain is a strong function of both temperature and bias current
 - ➔ gain becomes unpredictable and unstable
 - Low input dynamic range limits small-signal gain
 - ➔ Voltage gain $A_v \approx -R_c/R_e$ rather than BJT's intrinsic characteristics







- Transfer Function Analysis
 - Identify Operation Conditions
 - Input / Output Impedance
 - Voltage Gain


	Definition	Expression with emitter degeneration	Exp. w/o emitter deg. ($R_e=0$)
Current Gain	$A_i = i_{out}/i_{in}$	β	β
Voltage Gain	$A_v = v_{out}/v_{in}$	$-\frac{\beta R_c}{r_{\pi} + (\beta + 1)R_e}$	$\approx -g_m R_c$
Input Impedance	$r_{in} = v_{in}/i_{in}$	$r_{\pi} + (\beta + 1)R_e$	r_{π}
Output Impedance	$r_{out} = v_{out}/i_{out}$	R_c	R_c

Week 3 Workshop Review: LTspice Simulation

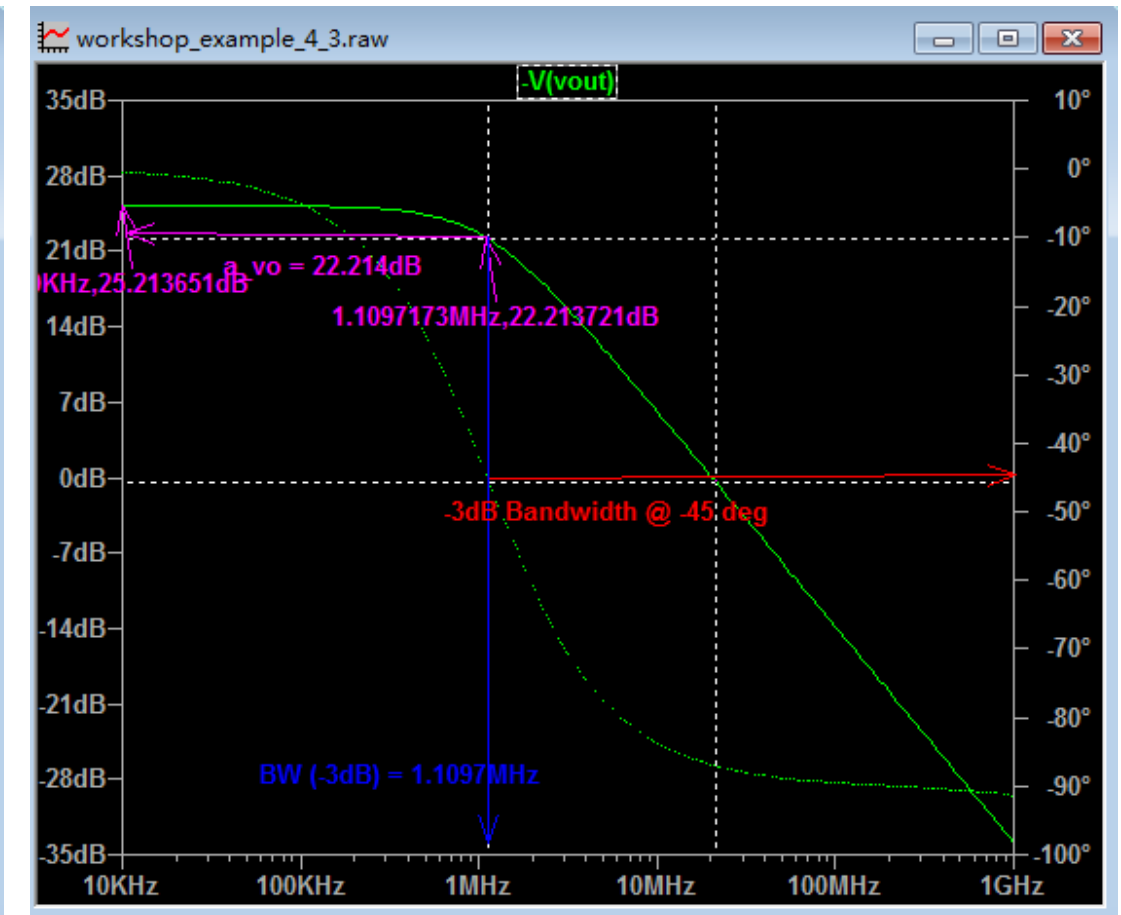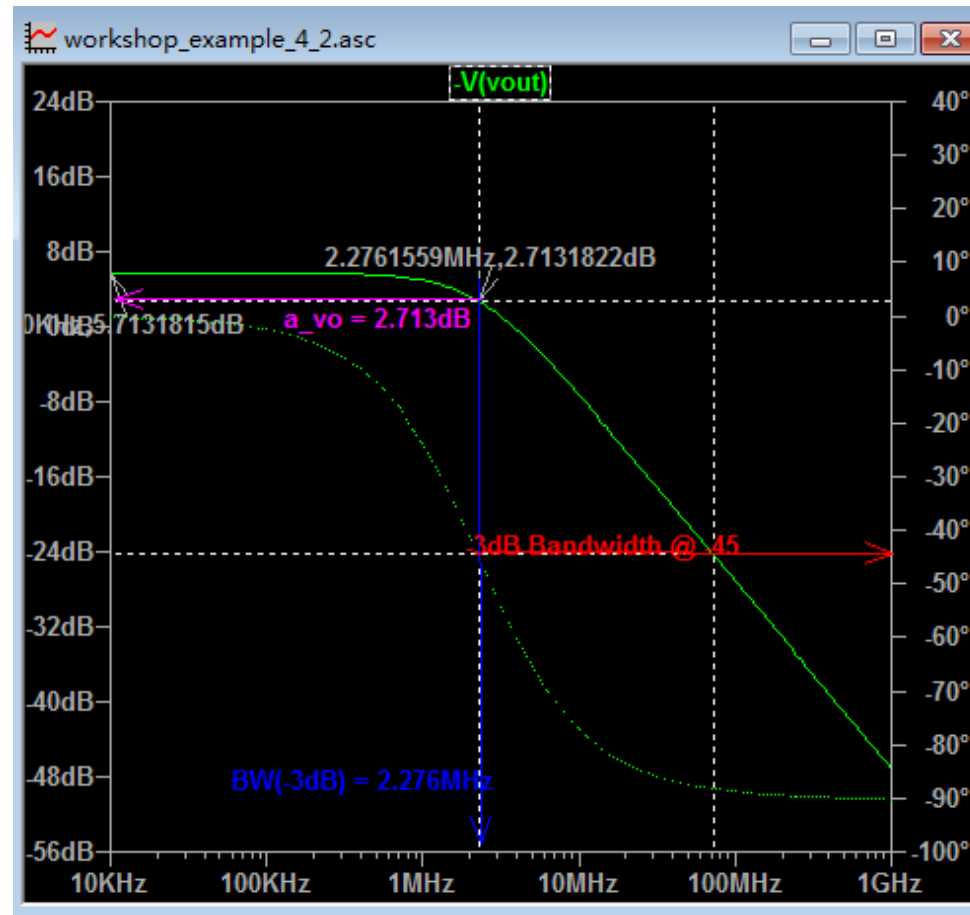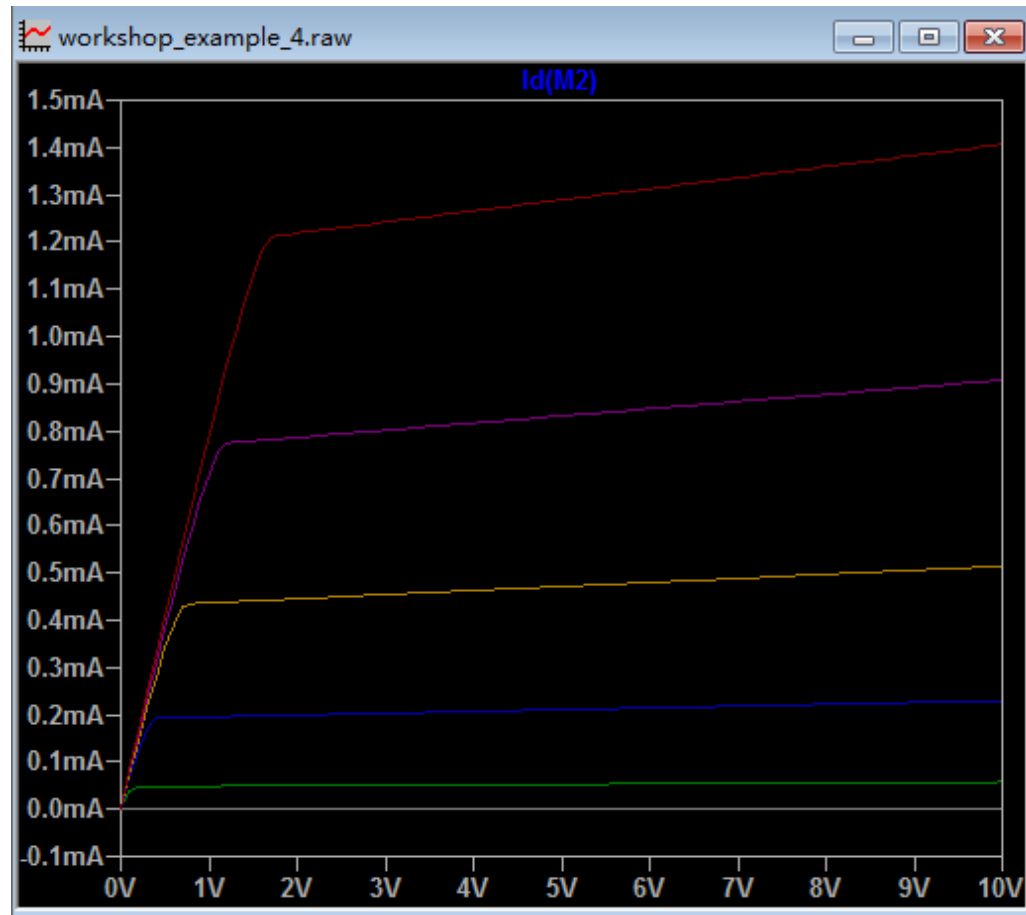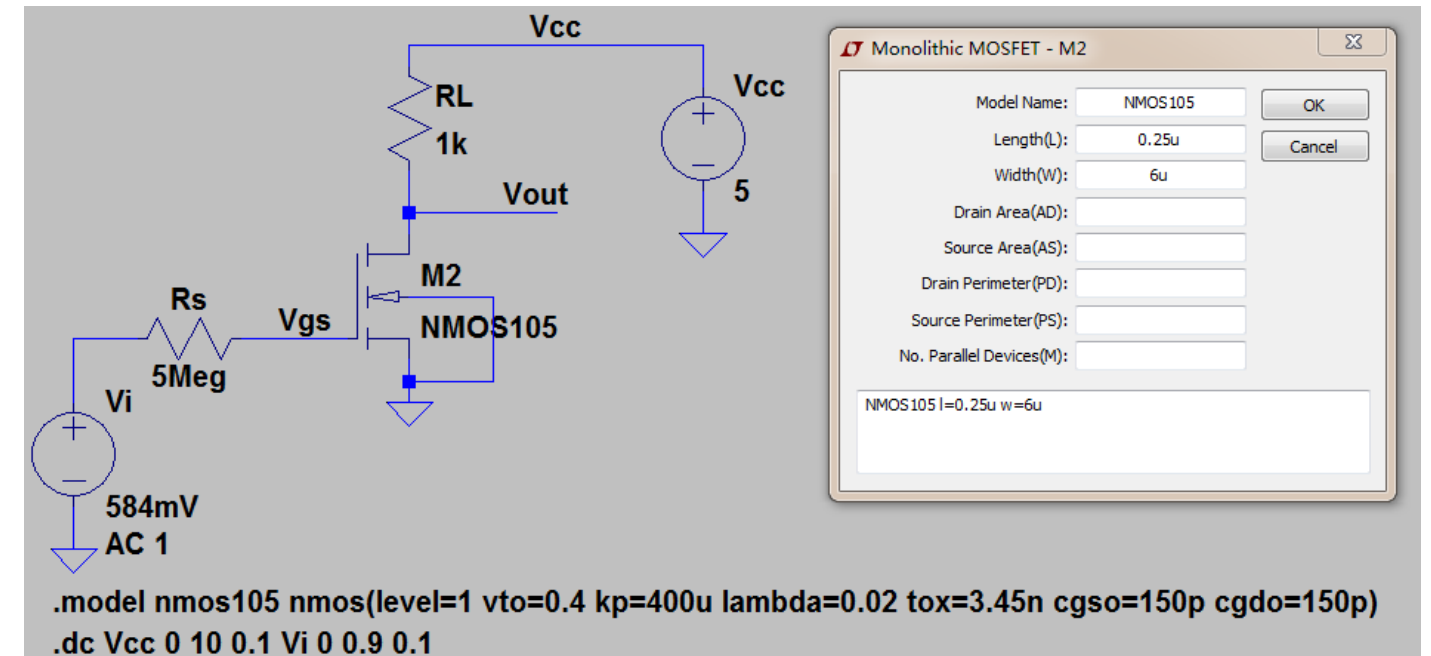- AC Analysis
 - Identify the operation conditions (voltage controlled device - Difference compare to BJT?)
 - Gain/Phase vs. frequency



Project Overview

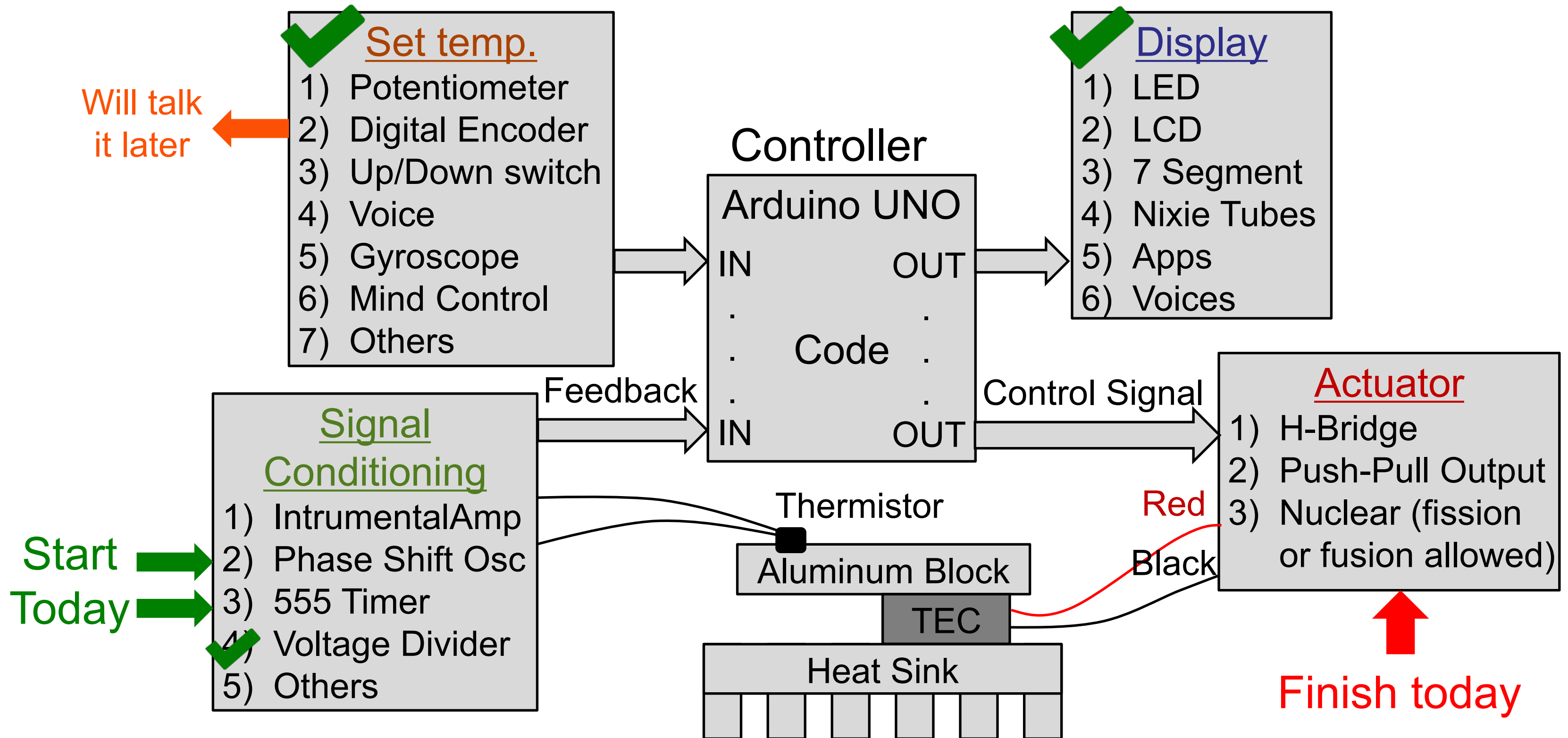


Drive the Actuator

High frequency/ current?



- H-bridge
 - PWM – Run simulation first!
 - Important: which transistor to pick (BC337!?)
- Push-Pull
 - PWM + LPF(what value to pick?)

bc337: max input current?

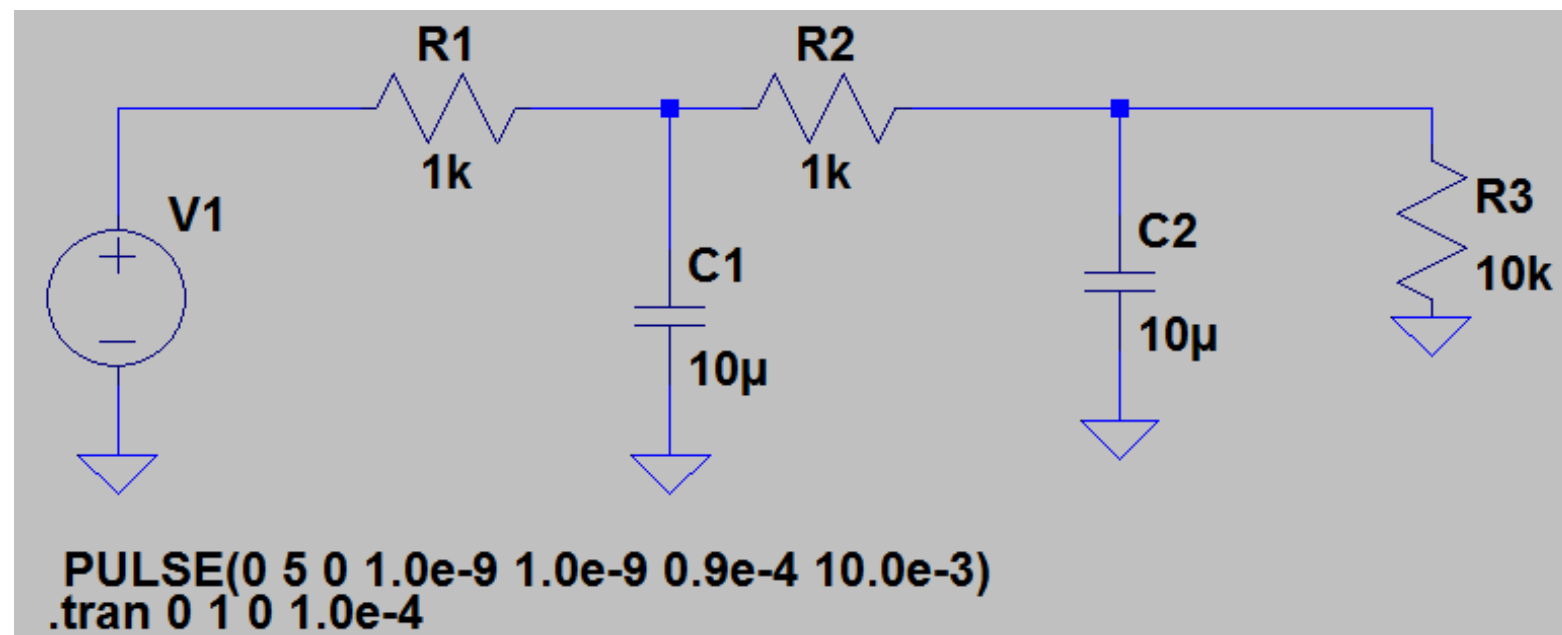

Push Pull; pnp&nnp
H-bridge:?

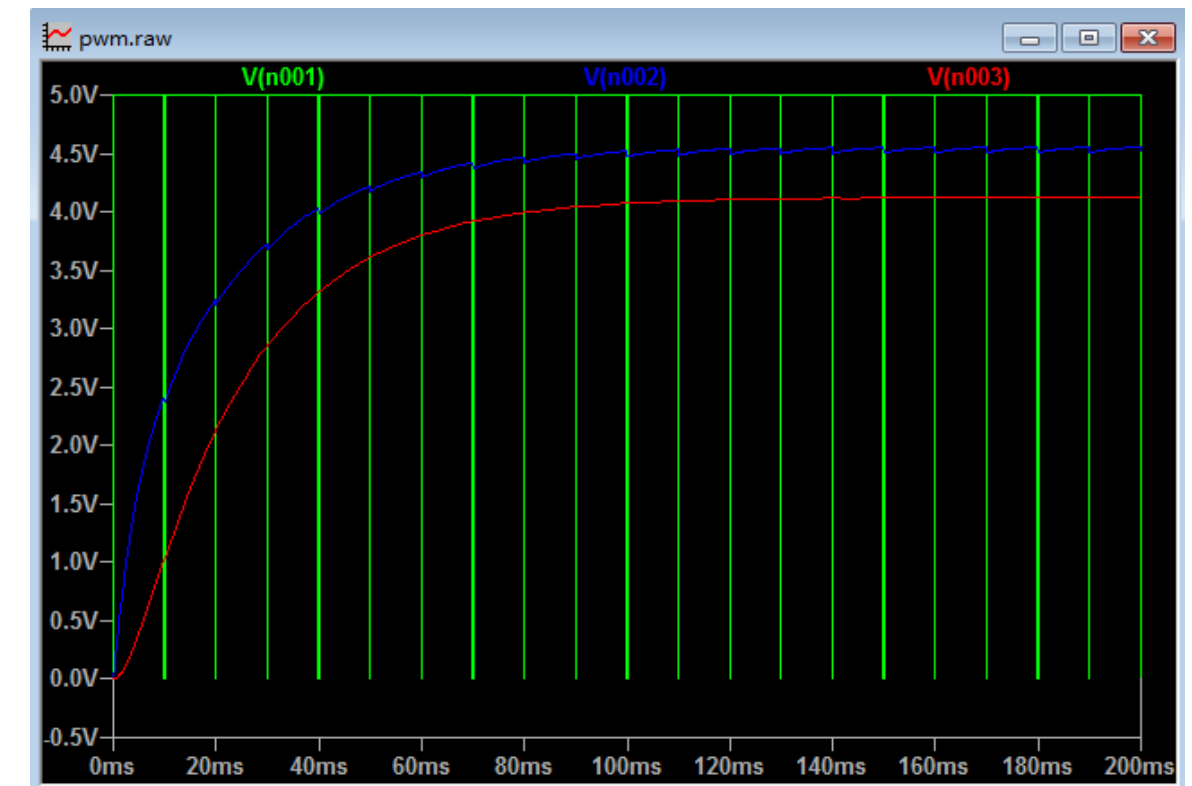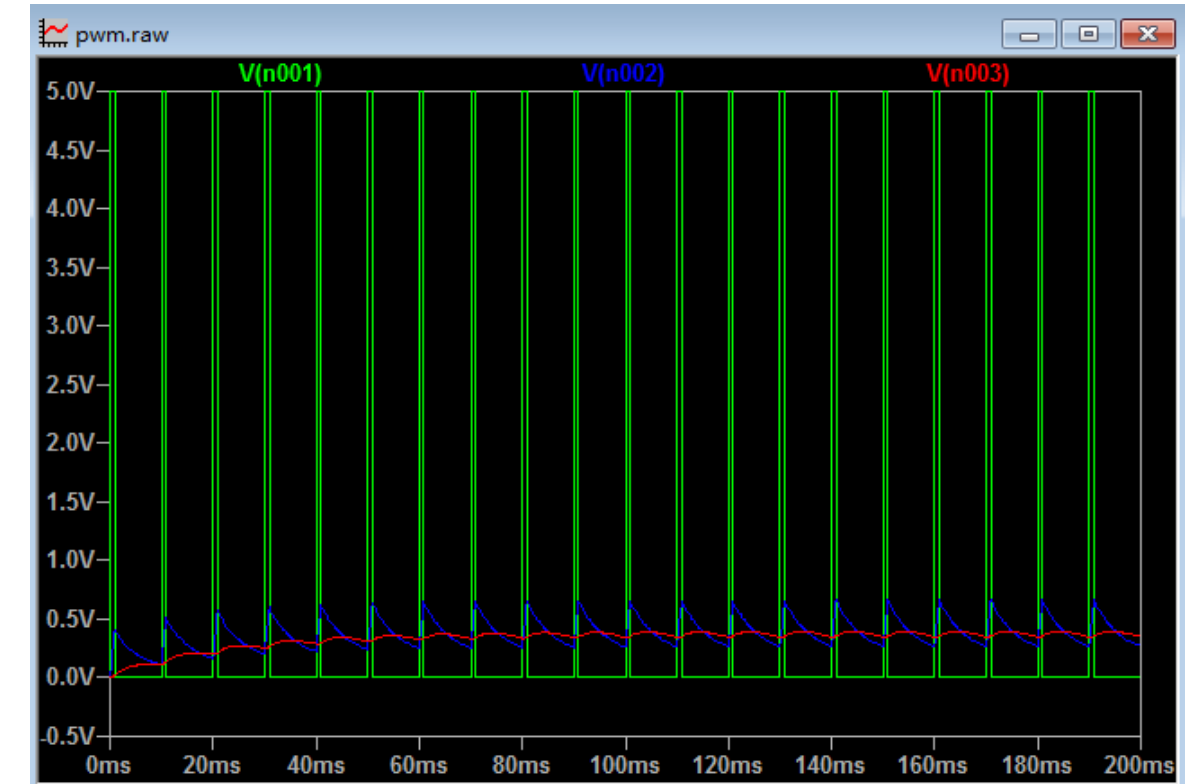- Which solution to pick
 - component counts, power consumption, accuracy, etc. which has less component? speed to change the temp?



Drive the Actuator using 555 Timer

- 555 timer can time from microseconds to hours
- Adjustable duty cycle
 - ➔ Modulated output based on input voltage


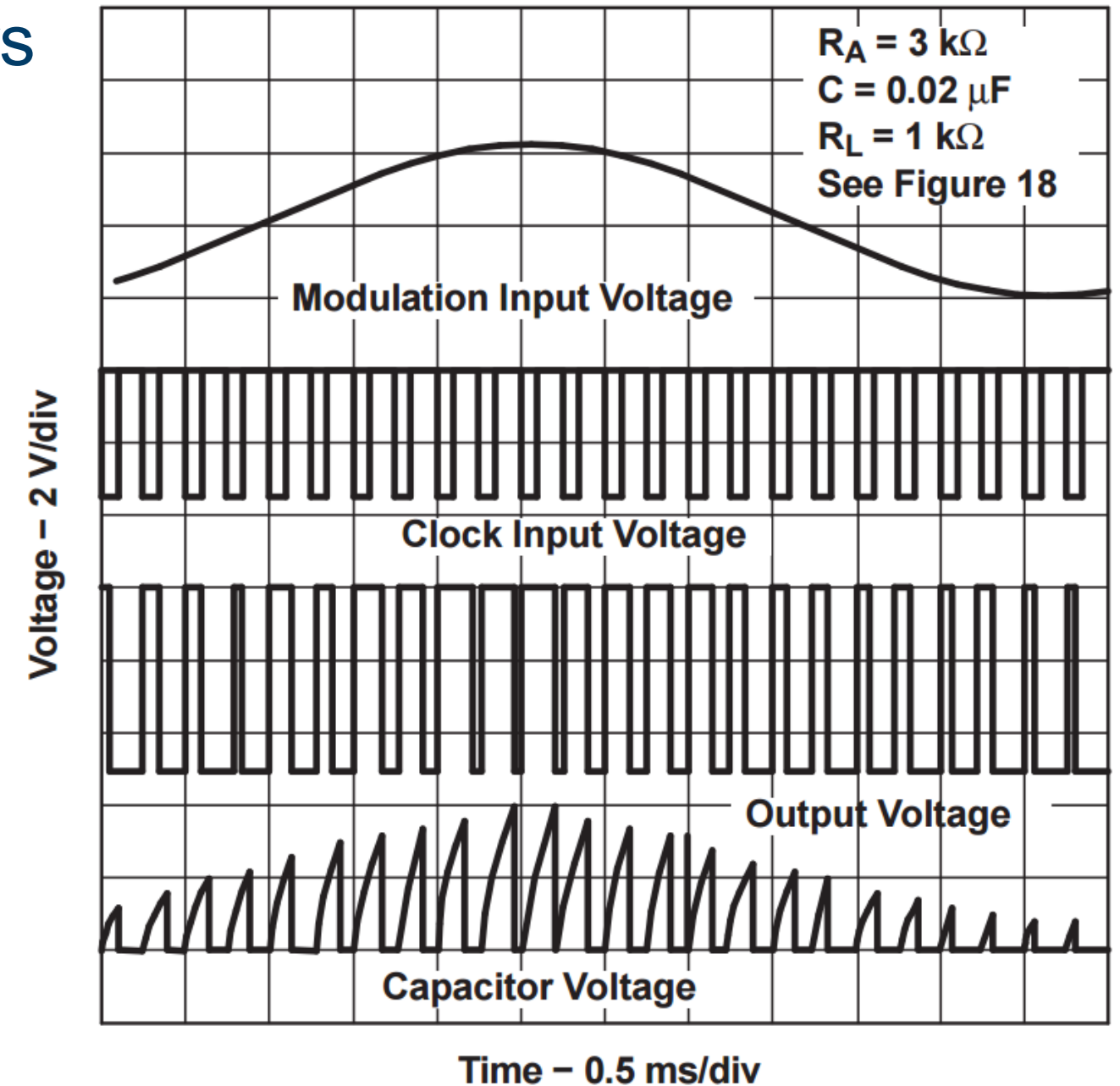
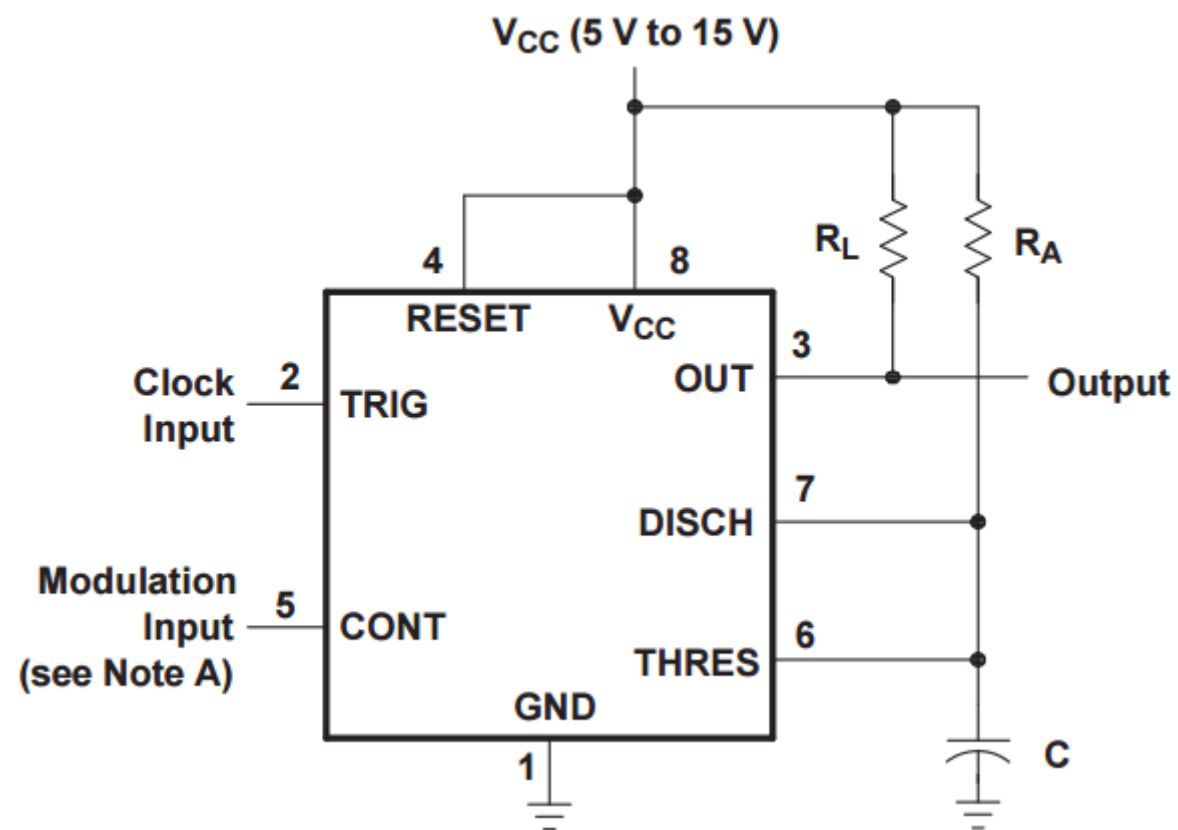


Figure 19. Pulse-Width-Modulation Waveforms




555 Timer

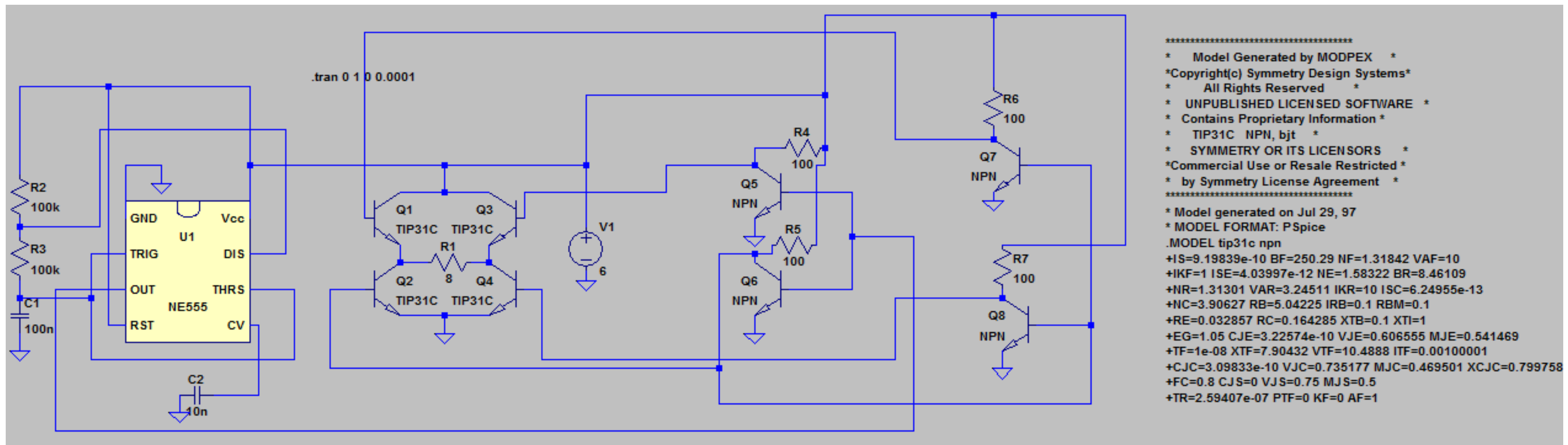- Can be used for both driving the actuator and signal conditioning




Phase Shift Oscillator

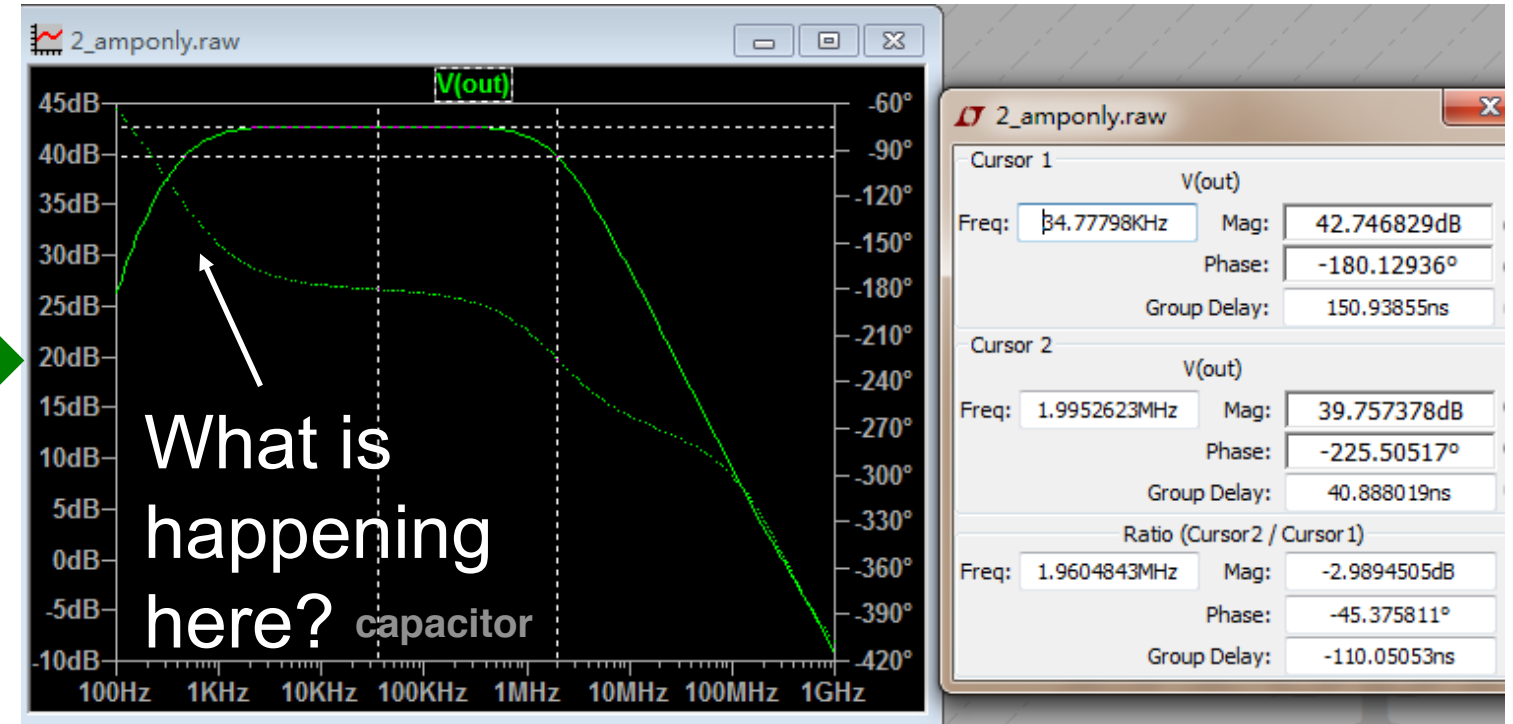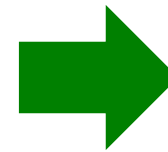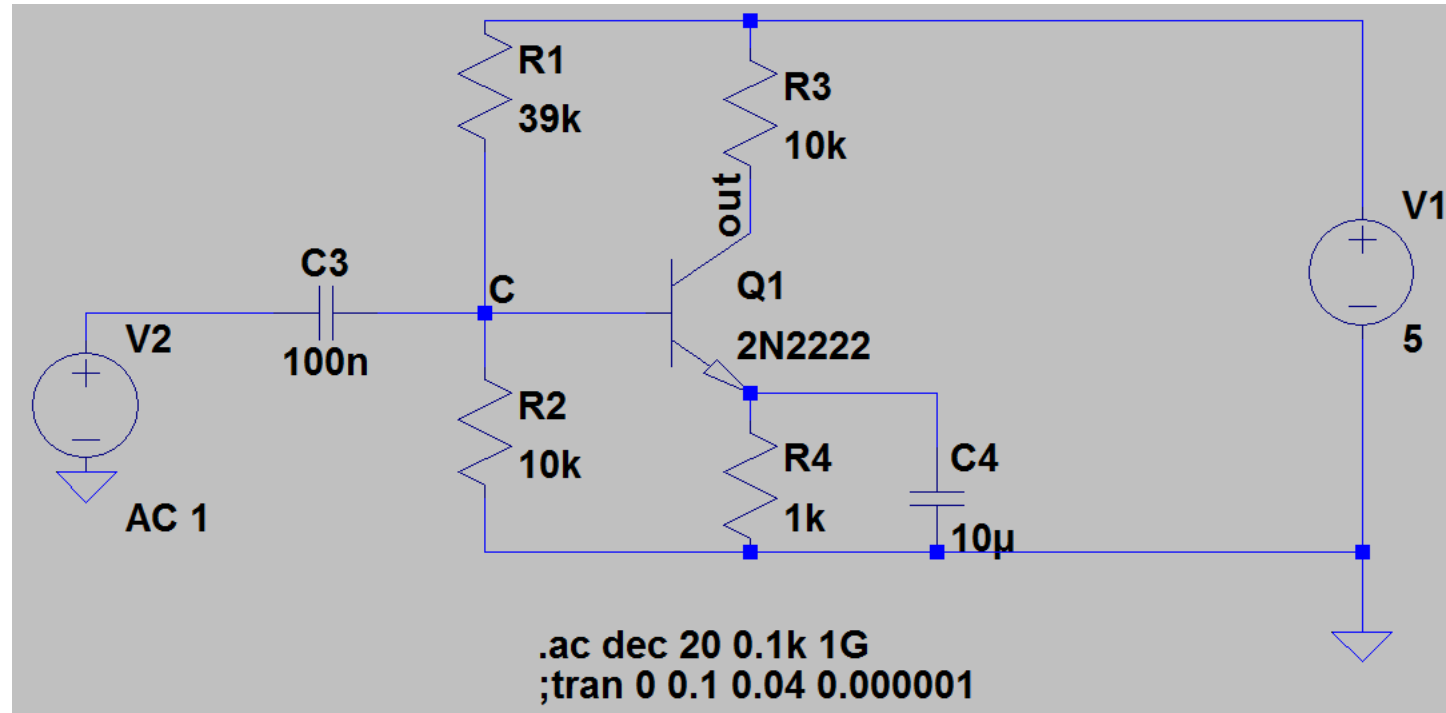
- Single stage CE BJT amplifier (Class A) \Rightarrow 180 phase shift (v_{out} vs v_{in})



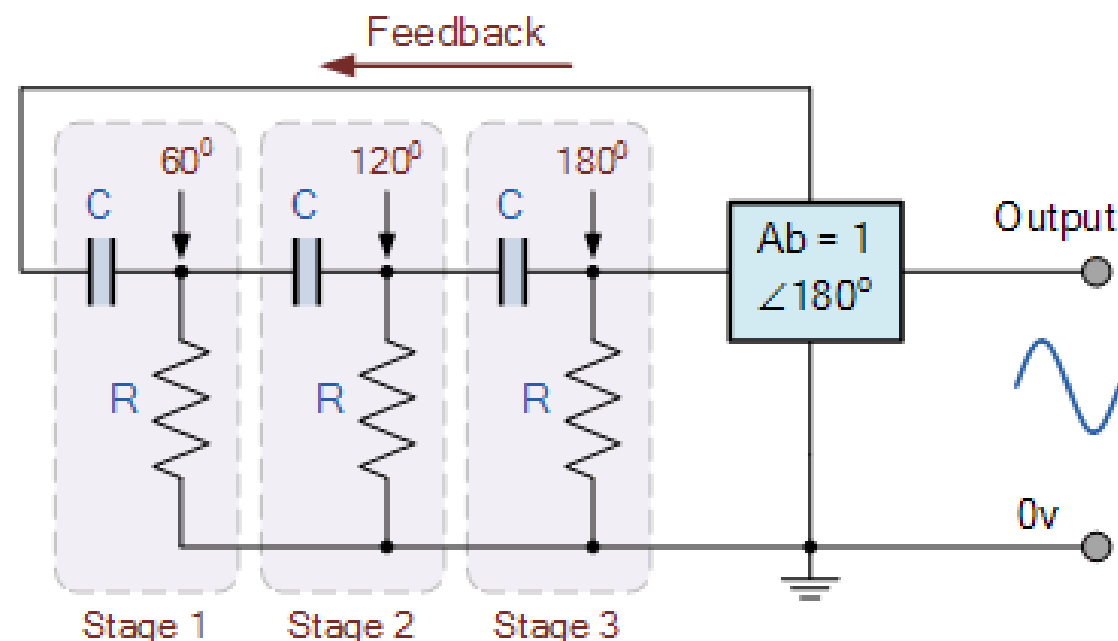- An oscillator \leftarrow sufficient feedback of the correct phase (i.e, “Positive Feedback”)



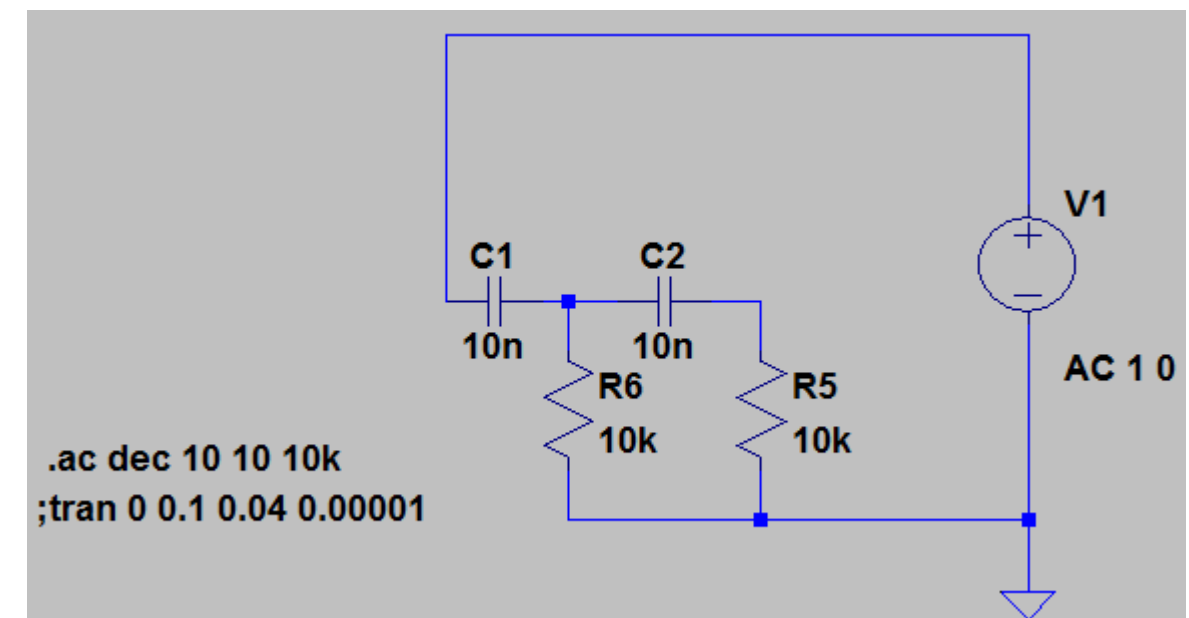Resistance-Capacitance Oscillator (RC Oscillator)



Phase Shift Oscillator

- RC Phase Angle:




- $X_C = \frac{1}{2\pi f C}, \quad R=R$

- $\rightarrow Z = \sqrt{R^2 + X_C^2}, \quad \phi = \tan^{-1} \frac{X_C}{R}$

- RC oscillator frequency

- $f_r = \frac{1}{2\pi RC\sqrt{2N}}$


- N: number of RC stages (i.e. 3)

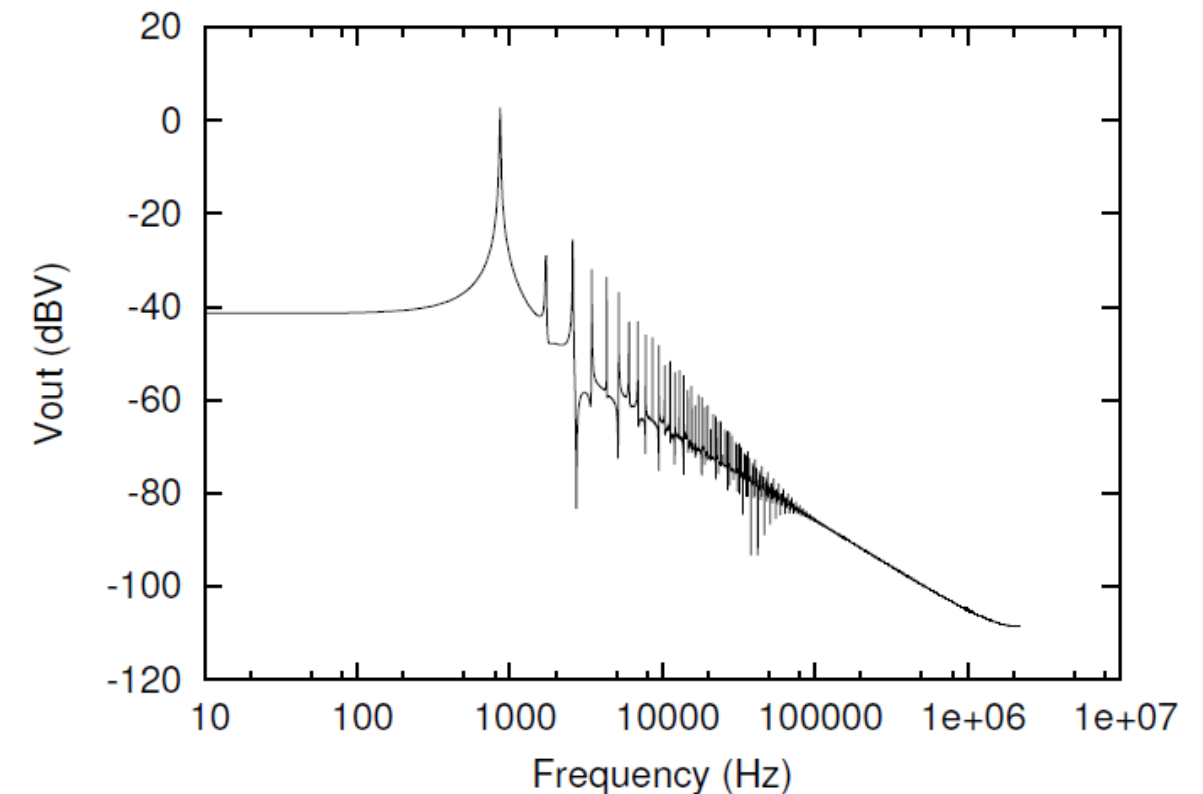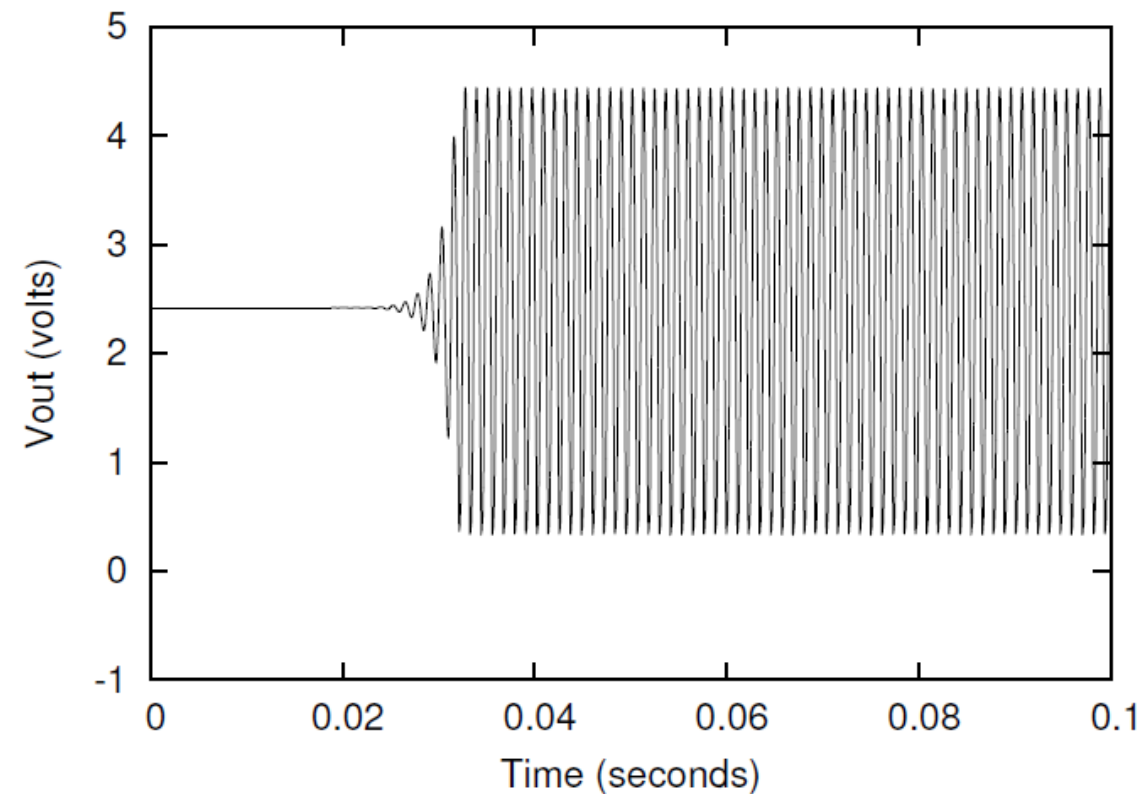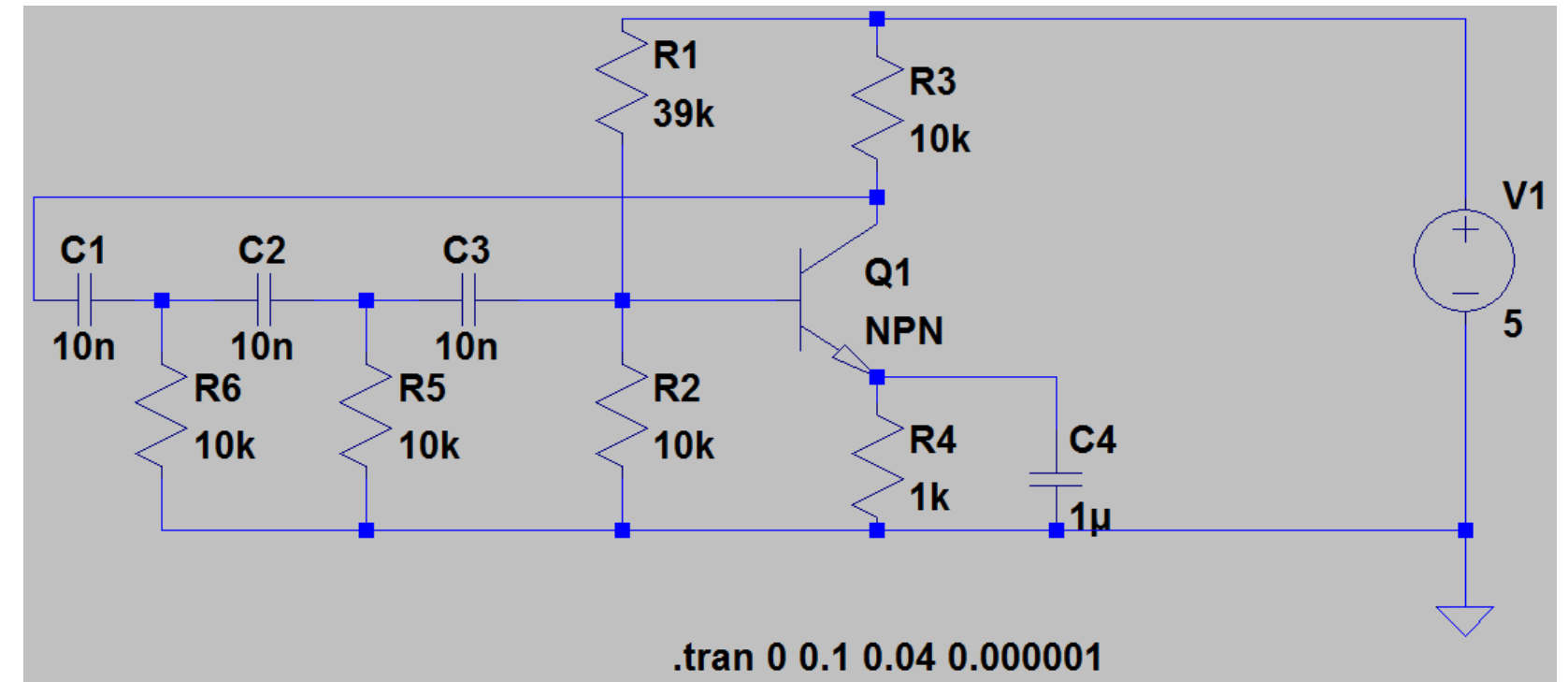

Phase Shift Oscillator

- Phase Shift Oscillator as temperature sensor
 - Replace R in filter section with a thermistor
 - Frequency and period become temperature dependent
 - Measure period using time for subsequent transitions to HIGH
 - How can we quantify quality of this measurement technique
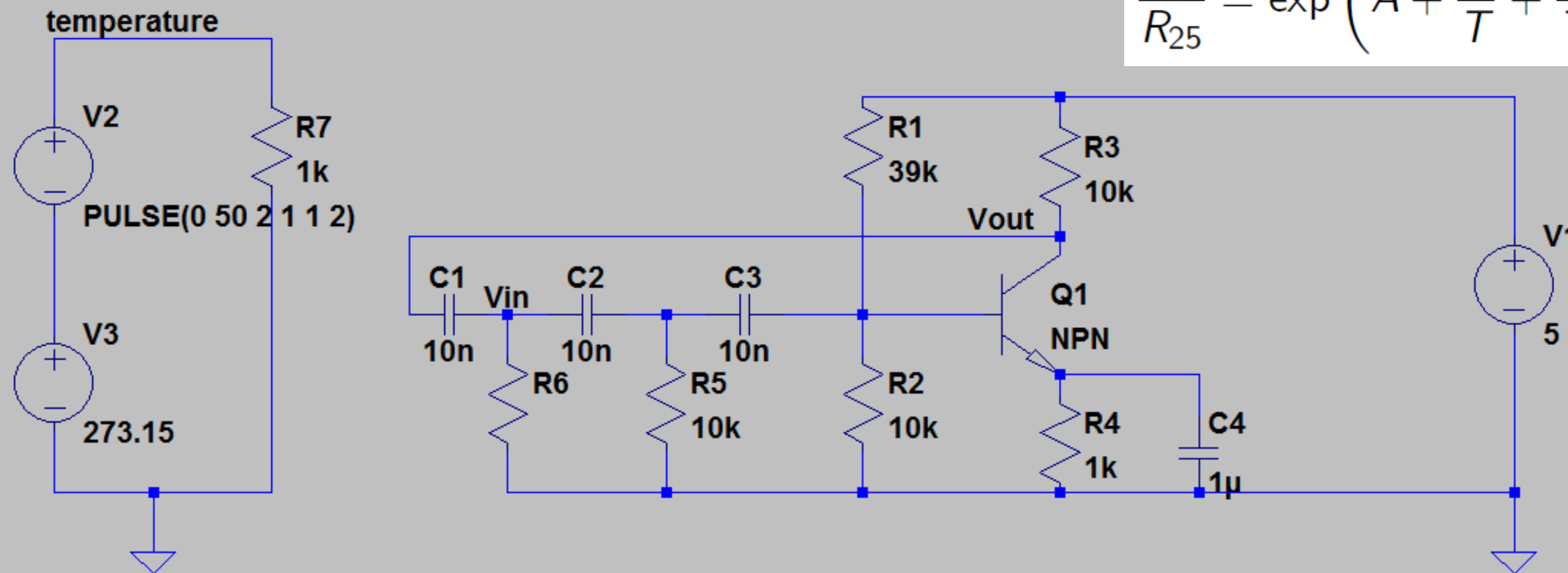
$$\frac{R_T}{R_{25}} = \exp \left(A + \frac{B}{T} + \frac{C}{T^2} + \frac{D}{T^3} \right)$$



.tran 0 3 2 0.00001

R=10000*exp(-14.141963+4430.783/V(temperature)-34078.983/V(temperature)/V(temperature)-8894192.9/V(temperature)/V(temperature)/V(temperature))