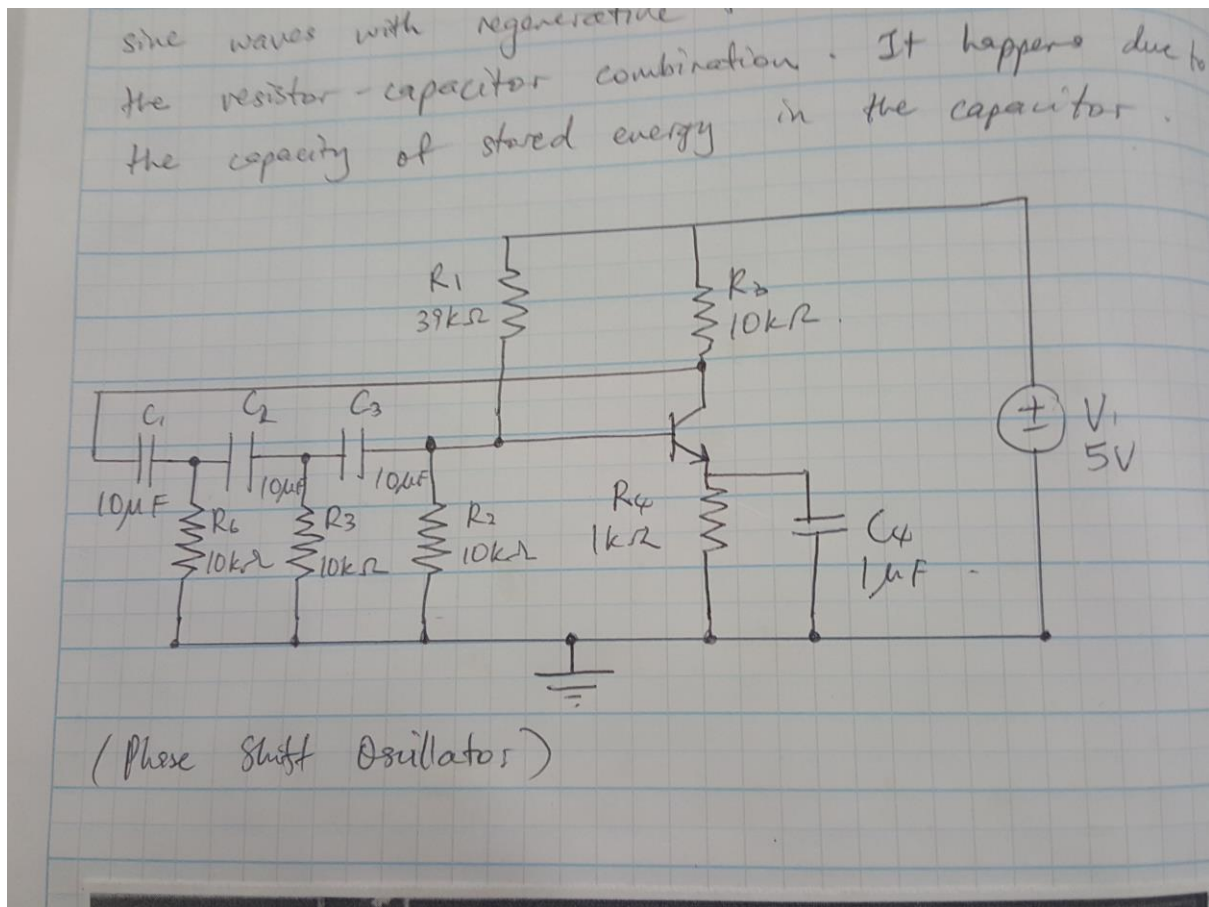



Workshop 4: Phase Shift Oscillator

The phase shift oscillator (PSO) is a circuit that creates sine waves with regenerative feedback obtained from the resistor-capacitor combination. It happens due to the capacity of stored energy in the capacitor.

PSO Diagrammmmmmmmm



Dr. Peter M. Farrell

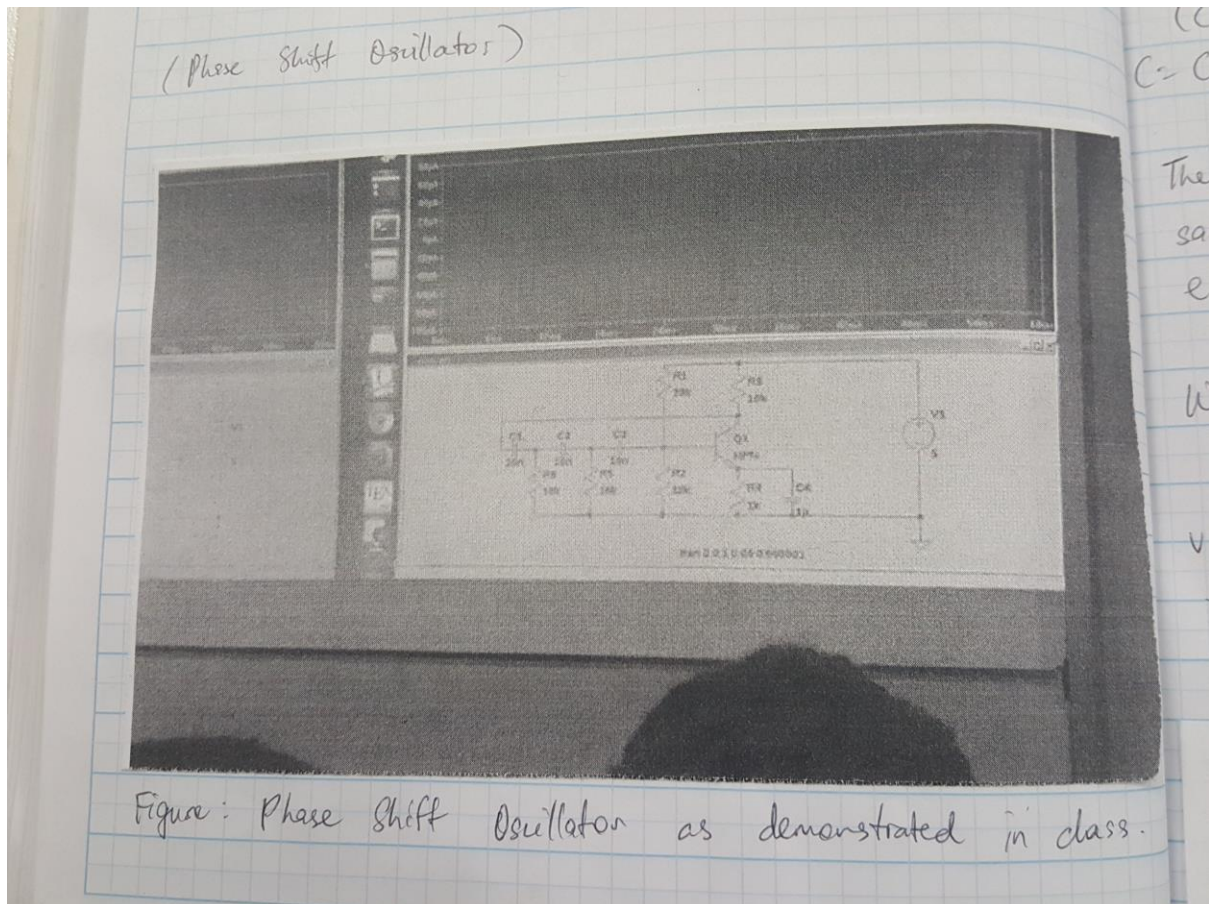


The above circuit shows the one we are to assemble. The transistor to be used is the BC548 (Datasheet attached). Could not determine manufacturer so assume it is Fairchild Conductors (as we needed to know pin orientations of transistor).

The PSO has a phase shift of 180 degrees, since each RC combination [(C1 and R6), (C2 and R5), (C3 and R2)] has a phase shift of 60 degrees if $C=C_1=C_2=C_3$ and $R_2=R_5=R_6=R$.

The circuit was simulated in LTSpice. Files may be located in emails.

We expect to have a result as follows.

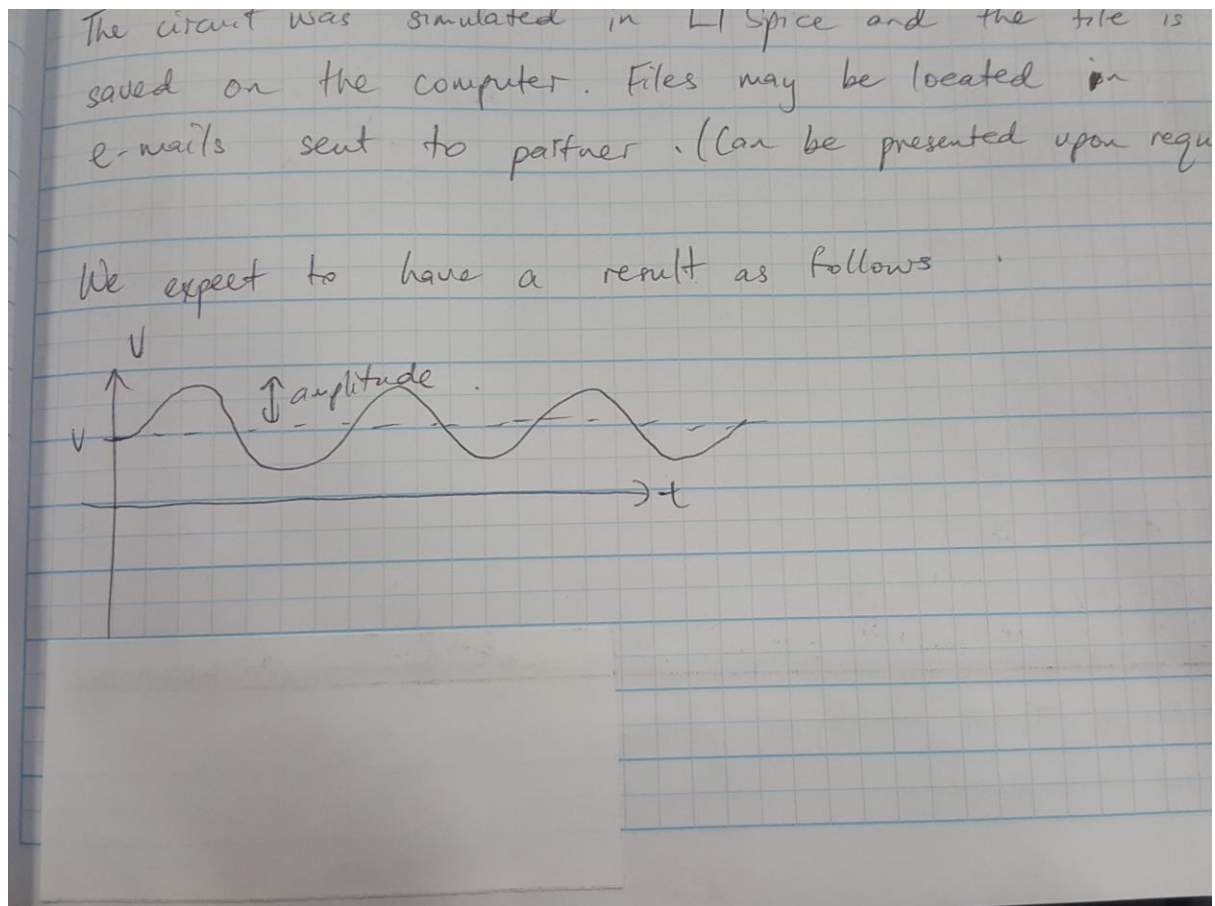

PICTUREEE

The PSO required a number of iterations to get it working right. Below shows the attempts to find the desired oscillations from the circuit.

V_B needs to be shifted towards the left in this case so increase the value of the resistor (i.e. 39kohms to 41kohms).

39kohms – sine wave with 3.9V

43kohms – good sine wave with a little clipping

Dr. Farrell suggests keeping the R value and continue with other aspects of PSO calibration.

Note: Oscilloscope used 10x and not 1x, hence gives distorted values and oscillations. Problems were fixed with the change. 1x gives good FFT.

PICUTRE

Figure: Noise in oscillations generated.


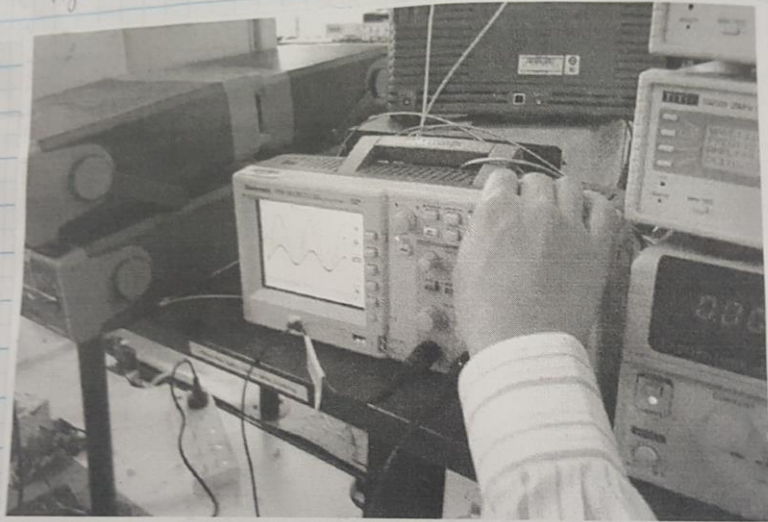


Figure: Tutor rectifying problems associated with oscillation generation.

Figure: h

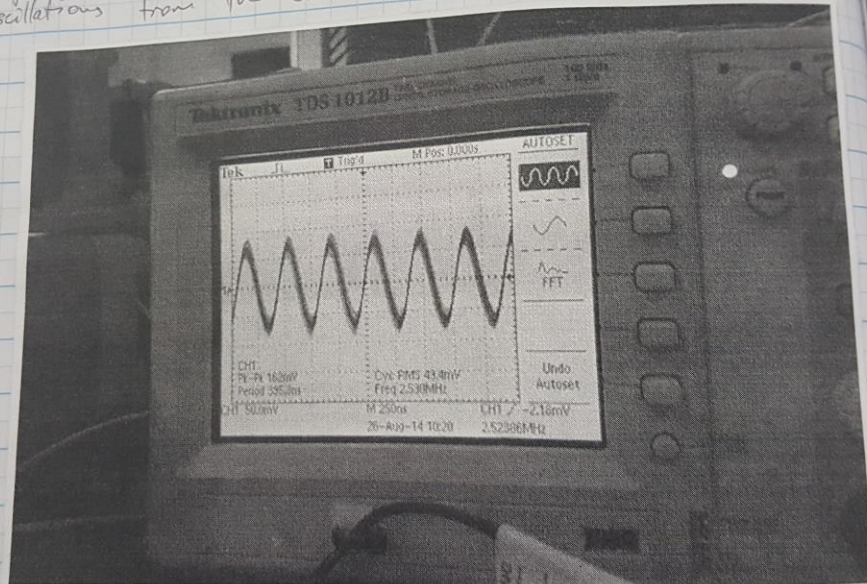The PSO required a number of iterations to get it work right. Below shows the attempts to find the desired oscillations from the circuit.



Note: Serial number of devices used are as follows:

DC Power Supply - EE 06546


Frequency Generator - EE 04897


Oscilloscope - TDS 1012B COS7264

Multimeter - 1110225866

$\rightarrow V_B$

be
adjusted to
desired V

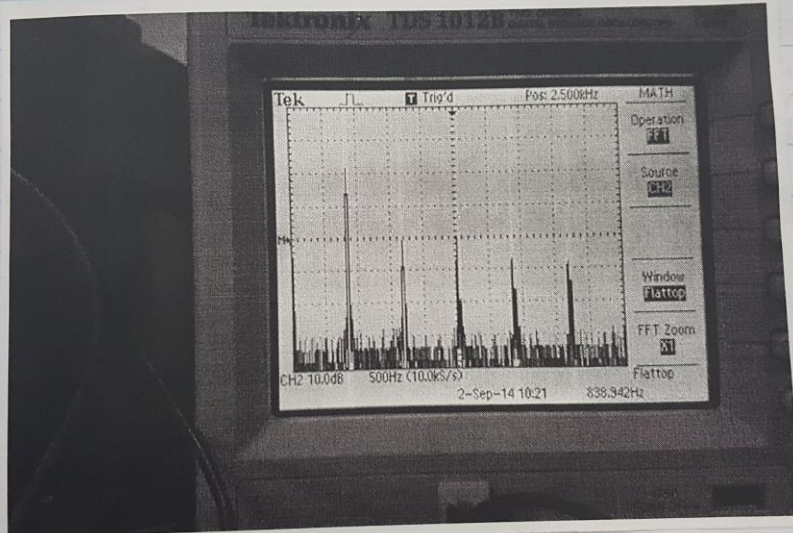

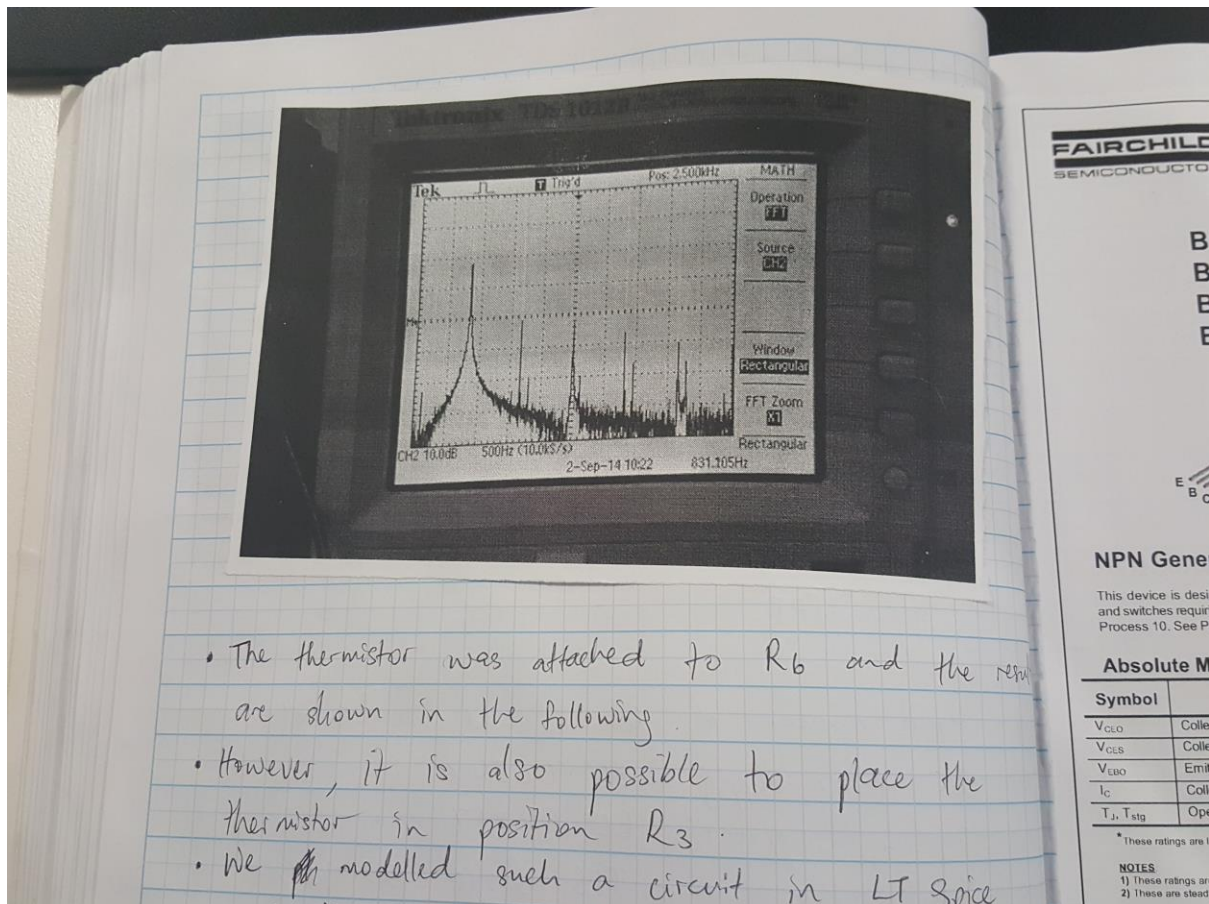

PCITRE FFT

- The thermistor was attached to R₆ and the results are shown in the following.
- However, it is also possible to place the thermistor in position R₃.
- We modelled such a circuit in LTSpice and it showed similar characteristics to the initial circuit.
- This LTSpice file can be found in Draft 14.

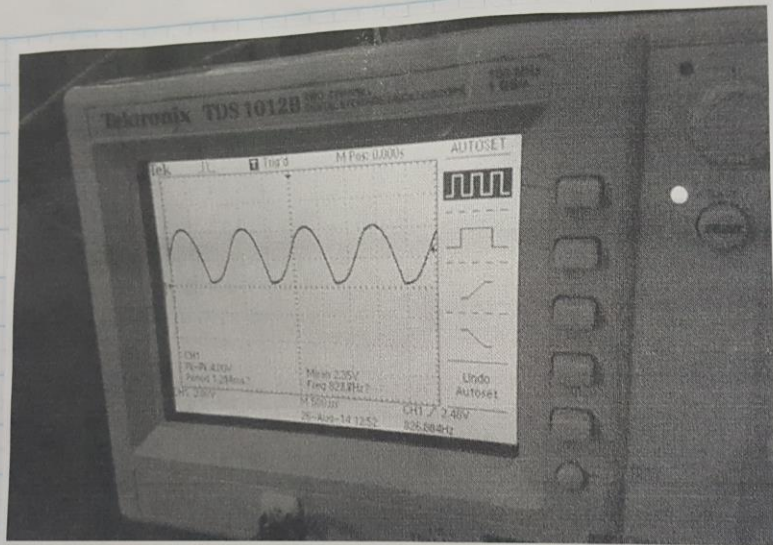


Figure: Oscillations generated by working phase Shift Oscillator

Notice that the sine waves are not exactly smooth.
 V_{out}

V_B needs
 30 inc

39 k Ω

43 k Ω




\Rightarrow Dr.
 conf

Note:

Note:

Figure: Oscillations generated by working phase Shift Oscillator

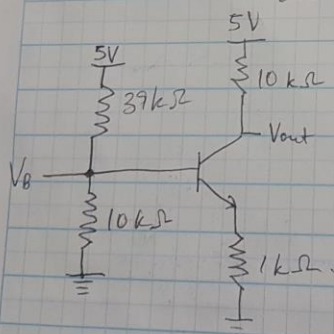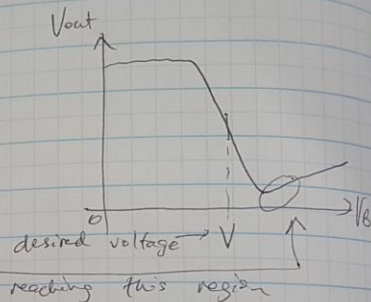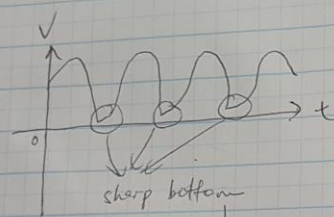Notice that the sine waves are not exactly smooth.



$$V_{out} = V_B \frac{10k}{10k + 39k}$$

\therefore can be
 adjusted to
 desired V

Note: Seri

DC

Freq


0

N

BC548 / BC548A / BC548B / BC548C

FAIRCHILD
SEMICONDUCTOR™

BC548
BC548A
BC548B
BC548C



TO-92

NPN General Purpose Amplifier

This device is designed for use as general purpose amplifiers and switches requiring collector currents to 300 mA. Sourced from Process 10. See PN 100A for characteristics.

Absolute Maximum Ratings* (TA = 25°C, unless otherwise noted)

Symbol	Parameter	Value	Units
V _{CEO}	Collector-Emitter Voltage	30	V
V _{CES}	Collector-Base Voltage	30	V
V _{BE0}	Emitter-Base Voltage	5.0	V
I _C	Collector Current - Continuous	500	mA
T _J , T _{stg}	Operating and Storage Junction Temperature Range	-55 to +150	°C

* These ratings are limiting values above which the semiconductor device may be impaired.

NOTES:

1) These ratings are based on a maximum junction temperature of 150 degrees C.

2) These are steady state limits. The device should be consulted on applications involving pulsed or low duty cycle operations.

Thermal Characteristics (TA = 25°C, unless otherwise noted)


Symbol	Characteristic	Max	Units
P _D	Total Device Dissipation Derate above 25°C	625	mW
R _{θJC}	Thermal Resistance, Junction to Case	85.0	mW/°C
R _{θJA}	Thermal Resistance, Junction to Ambient	200	°C/W

© 1997 Fairchild Semiconductor Corporation

544-ABC, Rev. B

NPN General Purpose Amplifier
(continued)

[illegible][illegible]

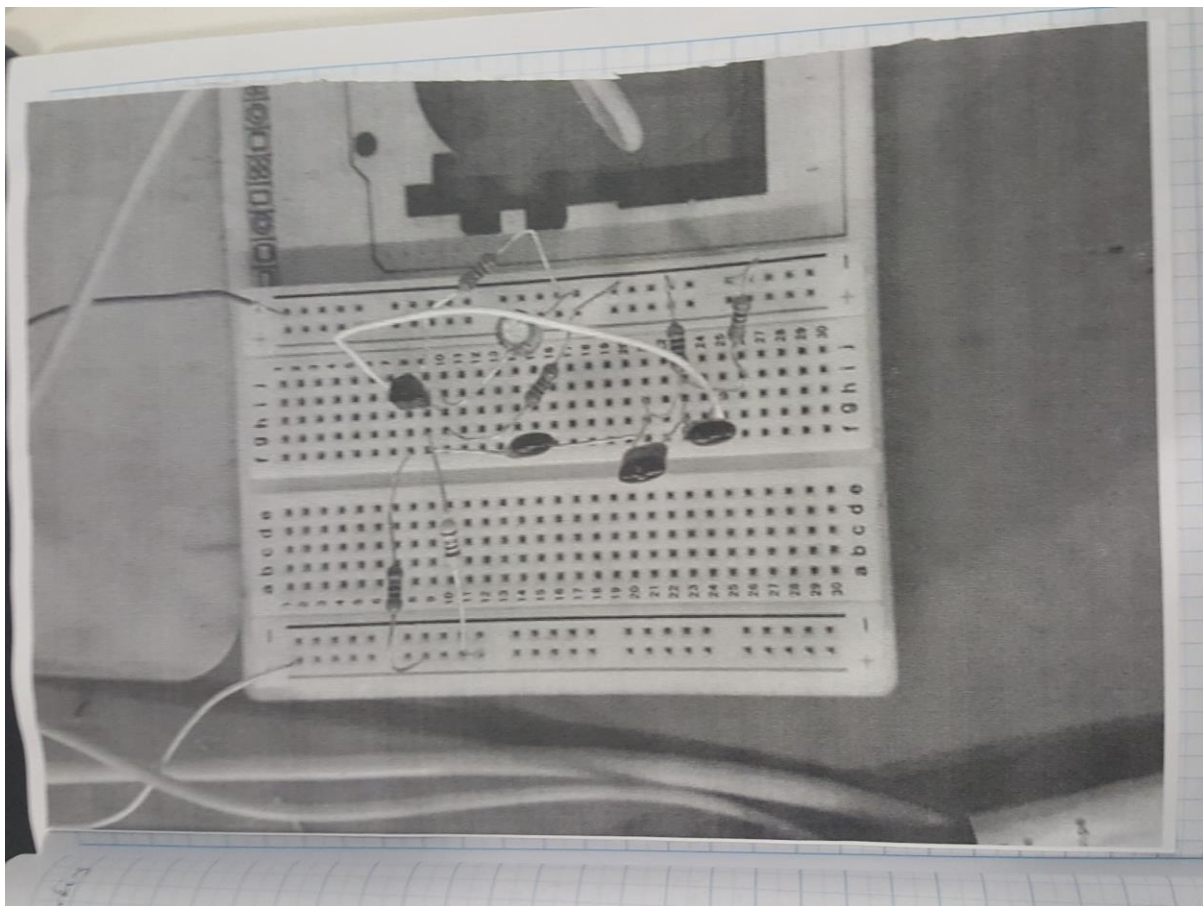

Workshop 5: Phase Shift Oscillator Calibration

2/9/2014

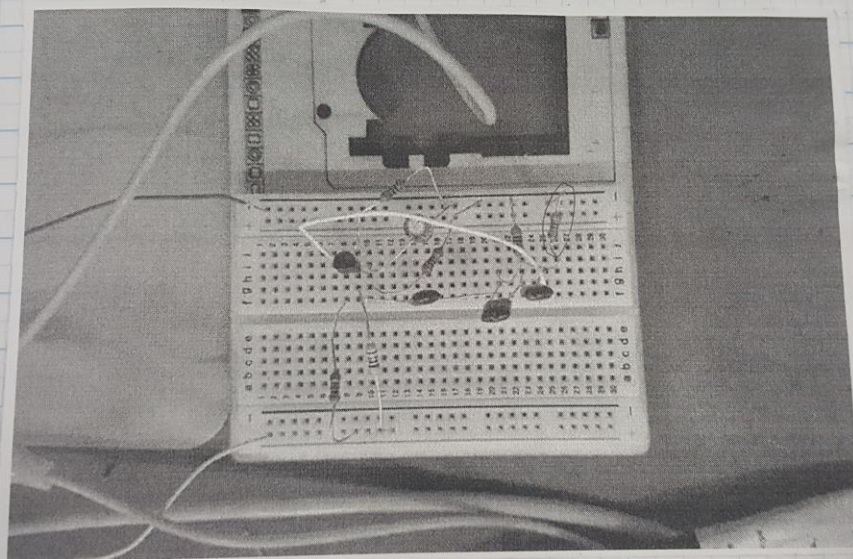


Figure: Phase Shift Oscillator from previous workshop.

In this workshop, we need to integrate the thermistor into the circuit and calibrate the phase shift oscillator. As such, the circled resistor is replaced with a thermistor and the circuit's frequency is calibrated in the Arduino such that it corresponds to a specific temperature. The formula used is:

$$1/T = A + B \log(R/R_{25}) + C (\log(R/R_{25}))^2 + D (\log(R/R_{25}))^3$$

Where A,B,C,D are the constants used in workshop 2

Procedure:

1. Choose random values of resistors (in the range 3kohms to 25kohms) based on the range of temperatures desired.
2. Connect the resistor to the point where the thermistor is supposed to be found.
3. Record the average of the frequencies using the Arduino.
4. Record resistance and temperature in a table in Microsoft Excel.
5. Calculate T based on formula on previous page.
6. Plot T against R and find trendline.
7. Insert trendline (best fit line) equation into Arduino (calibration). Now rewrite code for Arduino so it outputs T.

Values of R chosen: 16kohms, 18kohms, 6.2 kohms, 9k 7.5k 18k 18k 22k 3.9k 16k 10k 12k 23k 9k 25k 6.7k 22k 13k 3.6k

[illegible]

EXCEL:LLLLLLLLLLLLLLLLLLLLLLLL

```

/* Read Period */

#include <math.h>
double alpha=0.1;
double T=0;
void setup() {

    /* Defining pin 3 as a input */
    pinMode(3, INPUT);
    Serial.begin(9600);
}

void loop() {

    /* The program do nothing until the input 3 be between HIGH and LOW */
    /* HIGH is equal to 3 or more Volts */
    while(digitalRead(3) == HIGH) {
        ;
    }
    /* LOW is equal to 2 or less Vols */
    while(digitalRead(3) == LOW) {
        ;
    }
    double t =micros();
    while(digitalRead(3) == HIGH){
        ;
    }
    while(digitalRead(3) == LOW) {
        ;
    }


    t =micros()-t;
    double f=1.0e6/t;
    T = (1.0-alpha)*T+alpha*(102.58*log(f) - 659.57);

    Serial.println(T);
    delay(1);
}

```

CODEEEEEEEEEEEEEEEEEEEEE

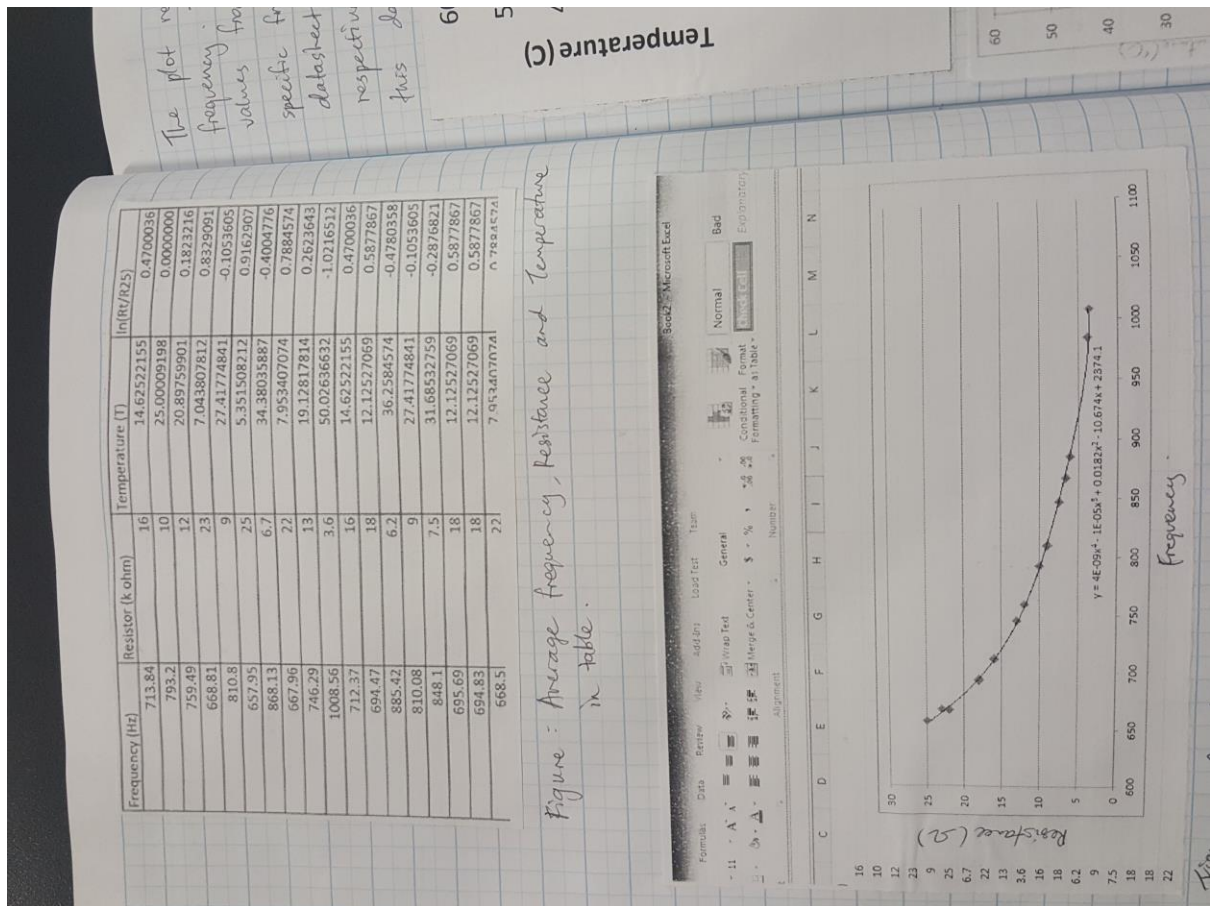The code gives the temperature of the measurement measured by thermistor. To calculate the temperature from frequency, resistance is correlated with frequency from the data and then the equation is used.



specific frequency. With the equation provided by the dataset of the thermistor, we calculated the respective temperature based on the resistance. With this data, we plotted the following plots.

The log function and quadratic equation both succinctly captures the relationship between temperature and frequency. Log. function chosen

Temperature (C)

Frequency

$y = -7E-05x^2 + 0.242x - 122.4$

$T = 102.58 \ln(x) - 659.57$

Log. function chosen

Frequency (Hz)

Time (s)

$r^2 = 102.58 \ln(x) - 659.57$

$y = 102.58 \ln(x) - 659.57$

Frequency (Hz)	Time (s)
650	10
660	12
670	15
680	18
690	22
700	25
750	35
800	45
850	55
900	65
950	75
1000	85
1050	95
1100	105

specific frequency. With the equation provided by the dataset of the thermistor, we calculated the respective temperature based on the resistance. With this data, we plotted the following plots.

The log function and quadratic equation both succinctly captures the relationship between temperature and frequency. Log. function chosen

Temperature (C)

Frequency

$y = -7E-05x^2 + 0.242x - 122.4$

$T = 102.58 \ln(x) - 659.57$

Log. function chosen

specific frequency. With the equation provided by the dataset of the thermistor, we calculated the respective temperature based on the resistance. With this data, we plotted the following plots.

The log function and quadratic equation both succinctly captures the relationship between temperature and frequency. Log. function chosen

Temperature (C)

Frequency

$y = -7E-05x^2 + 0.242x - 122.4$

$T = 102.58 \ln(x) - 659.57$

Log. function chosen

specific frequency. With the equation provided by the dataset of the thermistor, we calculated the respective temperature based on the resistance. With this data, we plotted the following plots.

The log function and quadratic equation both succinctly captures the relationship between temperature and frequency. Log. function chosen

Temperature (C)

Frequency

$y = -7E-05x^2 + 0.242x - 122.4$

$T = 102.58 \ln(x) - 659.57$

Log. function chosen

specific frequency. With the equation provided by the dataset of the thermistor, we calculated the respective temperature based on the resistance. With this data, we plotted the following plots.

The log function and quadratic equation both succinctly captures the relationship between temperature and frequency. Log. function chosen

Temperature (C)

Frequency

$y = -7E-05x^2 + 0.242x - 122.4$

$T = 102.58 \ln(x) - 659.57$

Log. function chosen

specific frequency. With the equation provided by the dataset of the thermistor, we calculated the respective temperature based on the resistance. With this data, we plotted the following plots.

The log function and quadratic equation both succinctly captures the relationship between temperature and frequency. Log. function chosen

Temperature (C)

Frequency

$y = -7E-05x^2 + 0.242x - 122.4$

$T = 102.58 \ln(x) - 659.57$

Log. function chosen

specific frequency. With the equation provided by the dataset of the thermistor, we calculated the respective temperature based on the resistance. With this data, we plotted the following plots.

The log function and quadratic equation both succinctly captures the relationship between temperature and frequency. Log. function chosen

Temperature (C)


Frequency

$y = -7E-05x^2 + 0.242x - 122.4$

$T = 102.58 \ln(x) - 659.57$

Log. function chosen

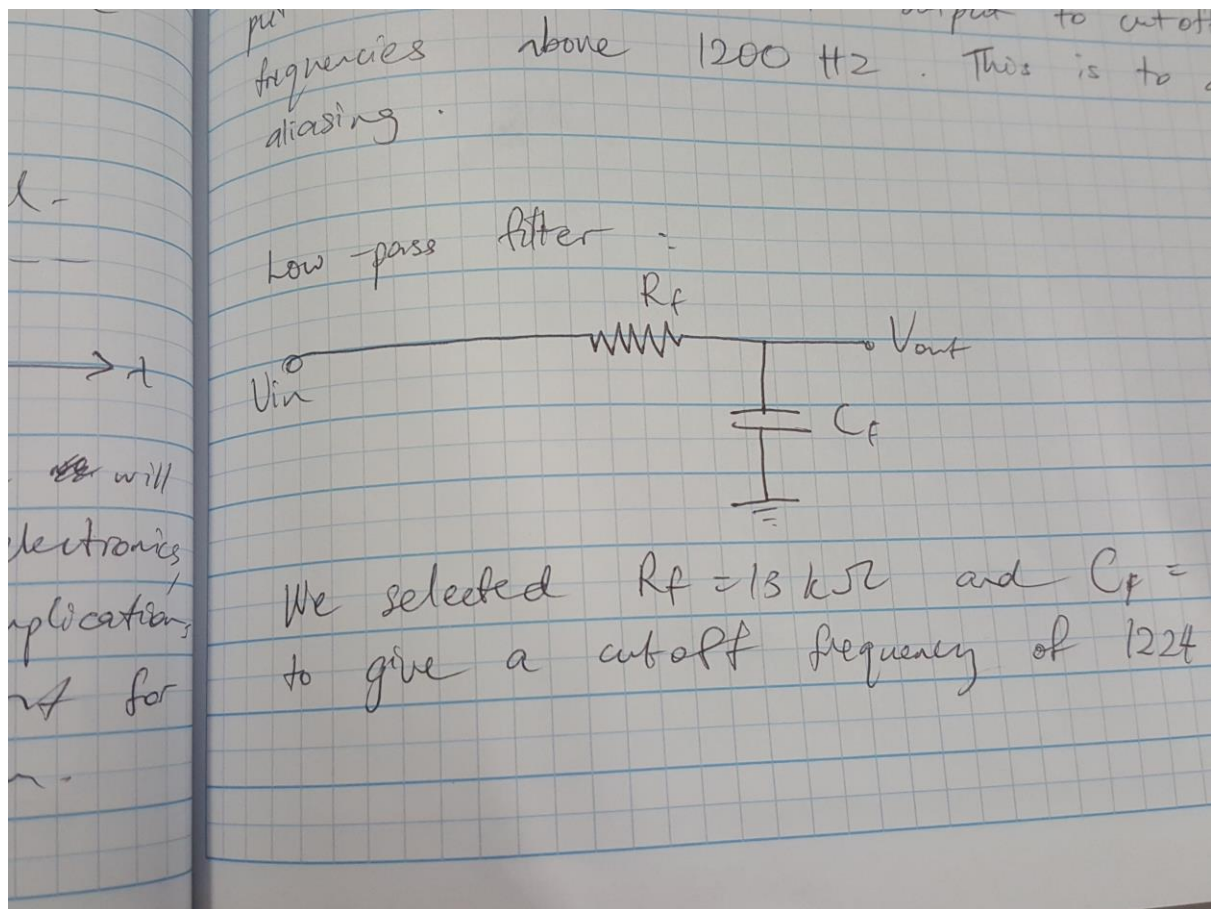We selected $R_F = 13 \text{ kohms}$, and $C_F = 10\text{nF}$ to give a cutoff frequency of 1224 Hz.



father: Nand Laganaga

Demonstrator: Nand Laganaga

Using the phase shift oscillator circuit in workshop 4
revised the circuit. Wires were better organized and
overall was neater. (Not like a bird's nest)


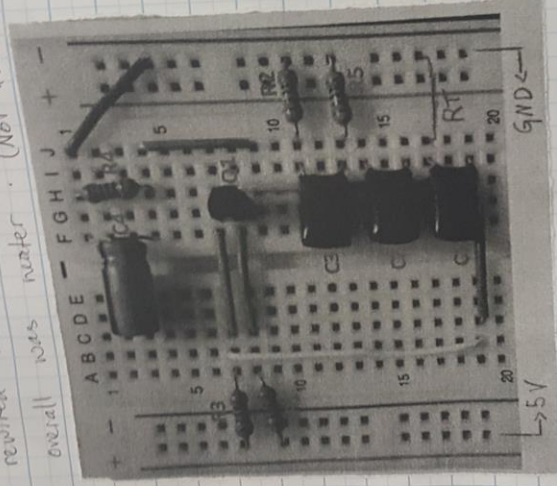


Figure: Phase shift

Oscillator Circuit

Table: Correlation between
resistance, frequency,
temperature and
 $\ln\left(\frac{R_T}{R_{25}}\right)$.

R(k Ω)	F(Hz)	T($^{\circ}$ C)	$\ln(R_T/R_{25})$
16000	729.37	14.6252	0.4700036
12000	778.48	20.8976	0.1823216
9100	832.75	27.1625	-0.0943107
24000	672.69	6.17771	0.8754687
3600	1030.13	50.0263	-1.0216512
3900	1018.18	47.93002	-0.9416085
7500	874.4	31.68533	-0.2876821
18000	711.42	12.1257	0.5877867
10000	813.73	25.00009	0.0000000
22000	684.48	7.953407	0.7884574
6800	897.16	34.02394	-0.3856625
6200	917.71	36.25846	-0.4780358
13000	765.07	19.12818	0.2623643
8200	856.67	29.58322	-0.1984509

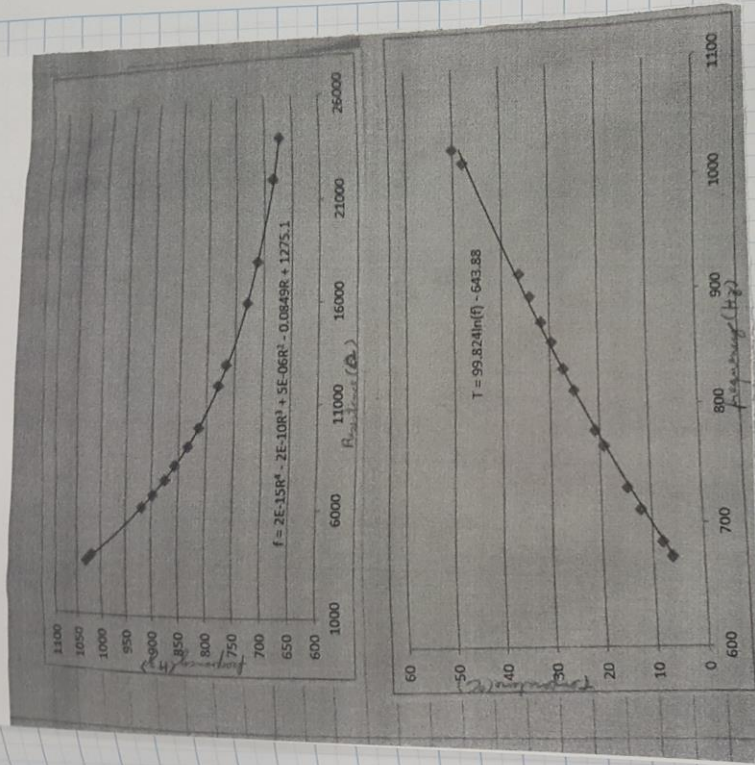

With this, we updated the code for the new equation

Code:

> Workshop Documents > Subjects > ES1 > Workshop 8 > W8c

Next, we deal with the display screen.